

FPGA-Optimised Uniform Random Number Generators using LUTs and Shift Registers

David B. Thomas and Wayne Luk
Imperial College London
{dt10,w.luk}@imperial.ac.uk

Achievements

- New FPGA-specific Random Number Generator (RNG)
 - Provide: hardware architecture + instantiation algorithm
- Architecture: use bit-wide LUTs and Shift Registers
 - Allow large period and good mixing (statistical quality)
 - Provide high clock rates with low resource utilisation
- Instantiation Algorithm: based on linear recurrences
 - Describe RNG instances using 5 parameters
 - Paper includes code generator and bit-exact simulator
- Complete RTL description of RNG instances
 - Open source VHDL available online


Motivation

- Monte-Carlo simulation works very well on FPGAs
 - Fine-grain parallelism: pipeline within simulator
 - Coarse-grain parallelism: instantiate parallel simulators
- Monte-Carlo is important, and becoming more so
 - Complex models often have no realistic analytical solution
 - Stochastic models can be much easier to describe
- But: Monte-Carlo is very sensitive to RNG quality
 - Obscure statistical biases can wreck simulation results
 - Parallel software guys are acutely aware of this
 - FPGA application designers need to take this into account
- Other applications also require good quality RNGs


Linear Feedback Shift Registers

- The “classic” hardware uniform RNG
 - Like a classic car: poor efficiency; tends to break down
- Known outside hardware as a “GFSR using XOR”
 - Usually prefixed by “For the love of god, don’t use a ...”
 - Largely discredited in the scientific software world
- Basic principles useful in most FPGA RNGs
 - Lets take a look...


LFSR: The Architecture

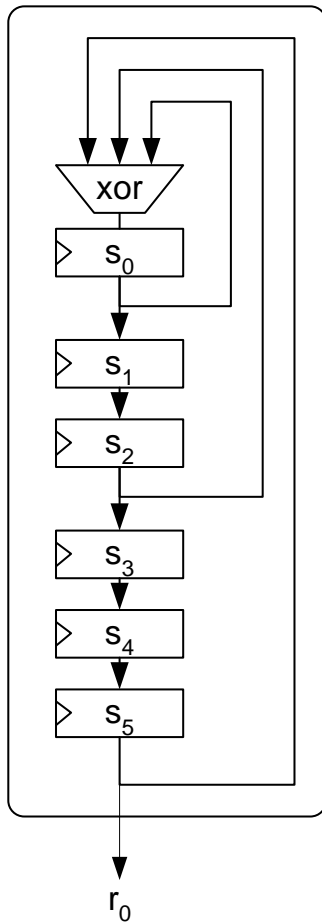


LFSR: The Architecture

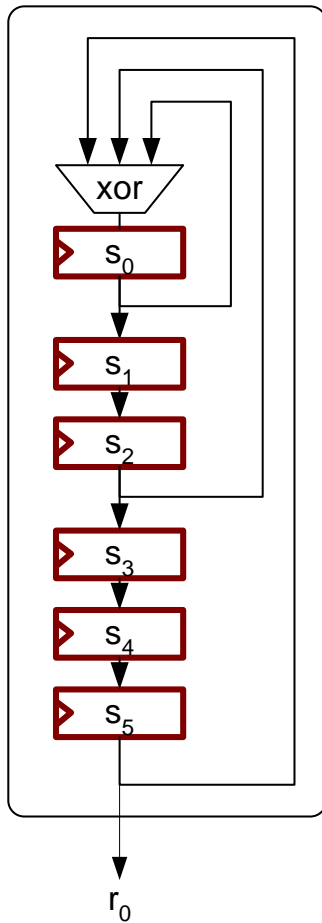


LFSR: The Architecture

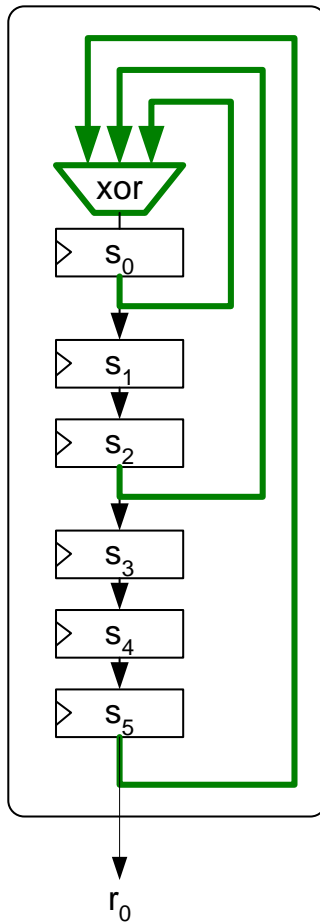

LFSR: The Architecture

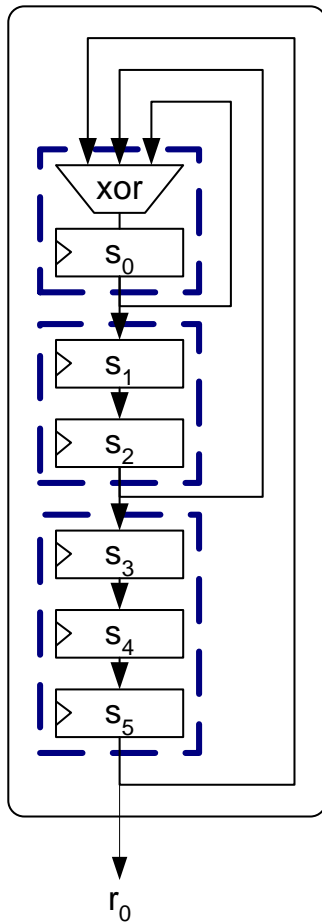


LFSR: The Theory

 

$$\mathbf{s}' = \mathbf{A} \times \mathbf{s}$$

$$\begin{bmatrix} s'_0 \\ s'_1 \\ s'_2 \\ s'_3 \\ s'_4 \\ s'_5 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 1 & 0 & 0 & 1 \\ 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 \end{bmatrix} \times \begin{bmatrix} s_0 \\ s_1 \\ s_2 \\ s_3 \\ s_4 \\ s_5 \end{bmatrix}$$


LFSR: The Theory

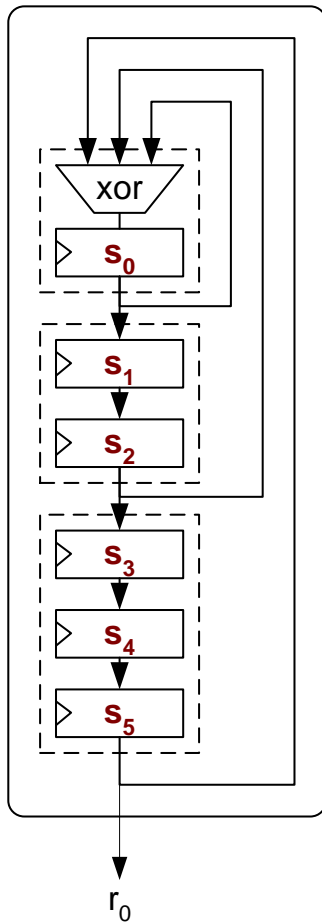

$$\mathbf{s}' = \mathbf{A} \times \mathbf{s}$$


$$\begin{bmatrix} s'_0 \\ s'_1 \\ s'_2 \\ s'_3 \\ s'_4 \\ s'_5 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 1 & 0 & 0 & 1 \\ 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 \end{bmatrix} \times \begin{bmatrix} s_0 \\ s_1 \\ s_2 \\ s_3 \\ s_4 \\ s_5 \end{bmatrix}$$

LFSR: The Theory

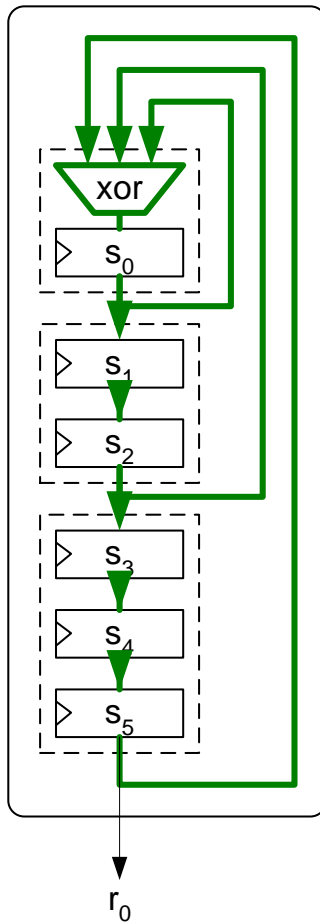


$$\begin{matrix}
 s'_0 \\
 s'_1 \\
 s'_2 \\
 s'_3 \\
 s'_4 \\
 s'_5
 \end{matrix}
 =
 \begin{bmatrix}
 1 & 0 & 1 & 0 & 0 & 1 \\
 1 & 0 & 0 & 0 & 0 & 0 \\
 0 & 1 & 0 & 0 & 0 & 0 \\
 0 & 0 & 1 & 0 & 0 & 0 \\
 0 & 0 & 0 & 1 & 0 & 0 \\
 0 & 0 & 0 & 0 & 1 & 0
 \end{bmatrix}
 \times
 \begin{matrix}
 s_0 \\
 s_1 \\
 s_2 \\
 s_3 \\
 s_4 \\
 s_5
 \end{matrix}$$


LFSR: The Theory

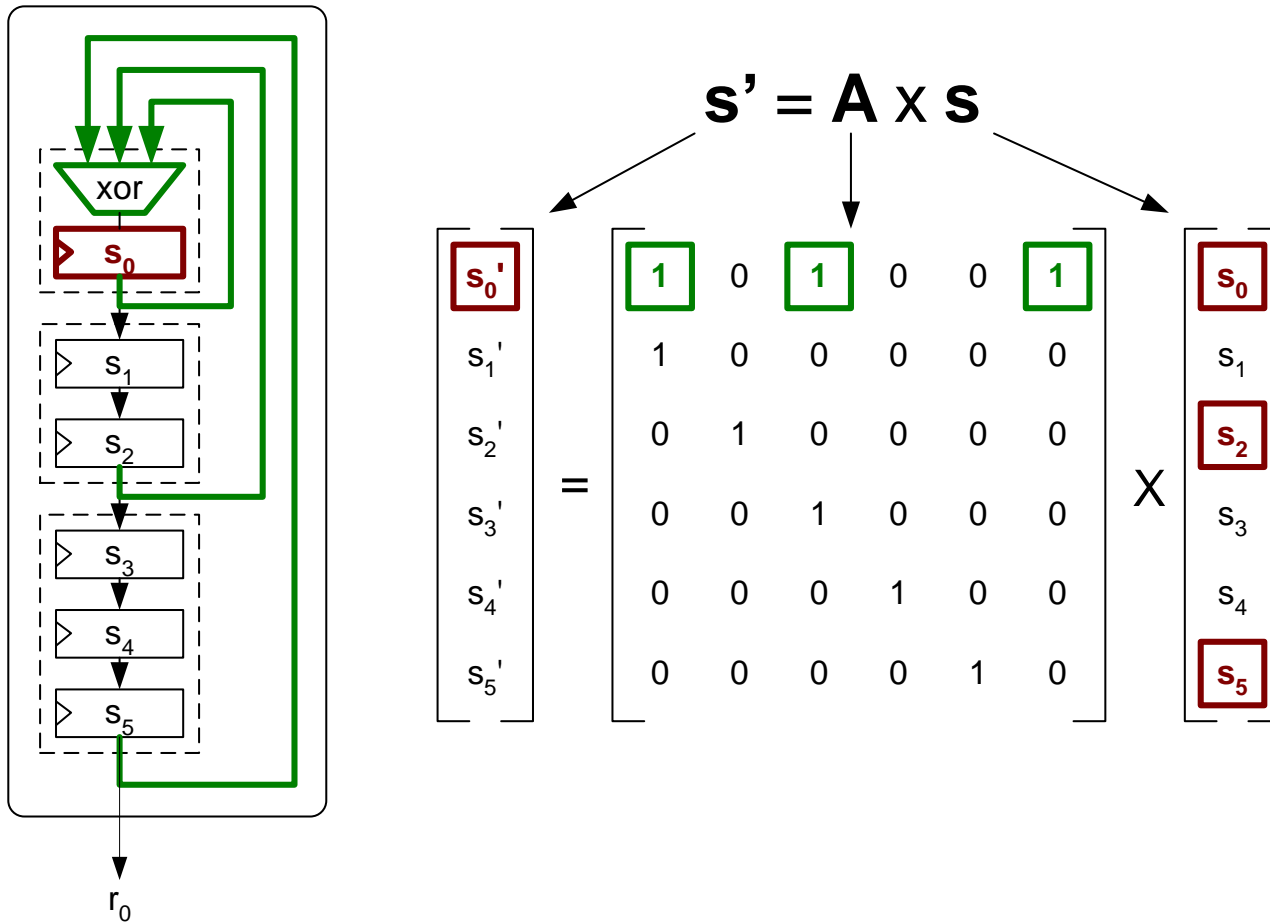

LFSR: The Theory

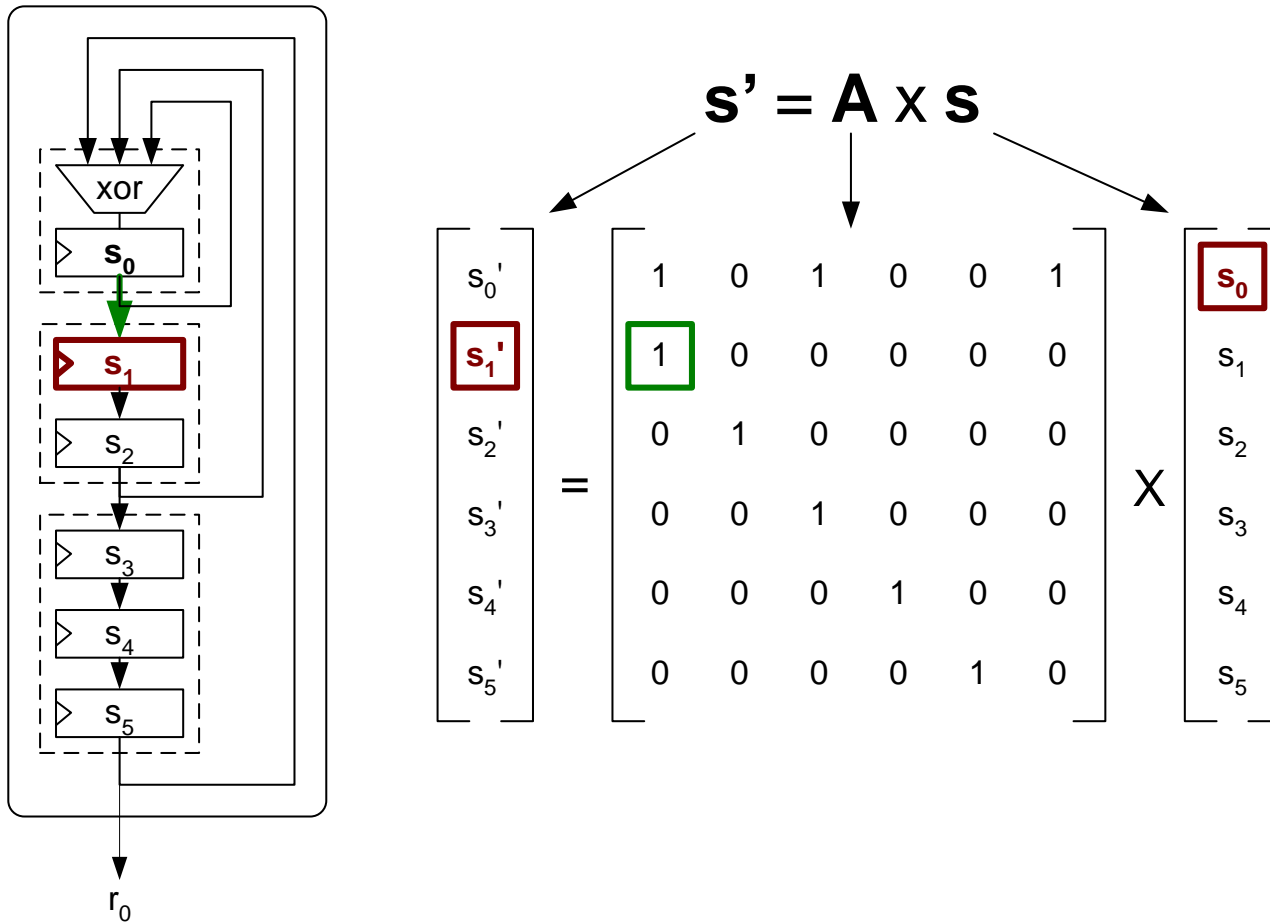

LFSR: The Theory

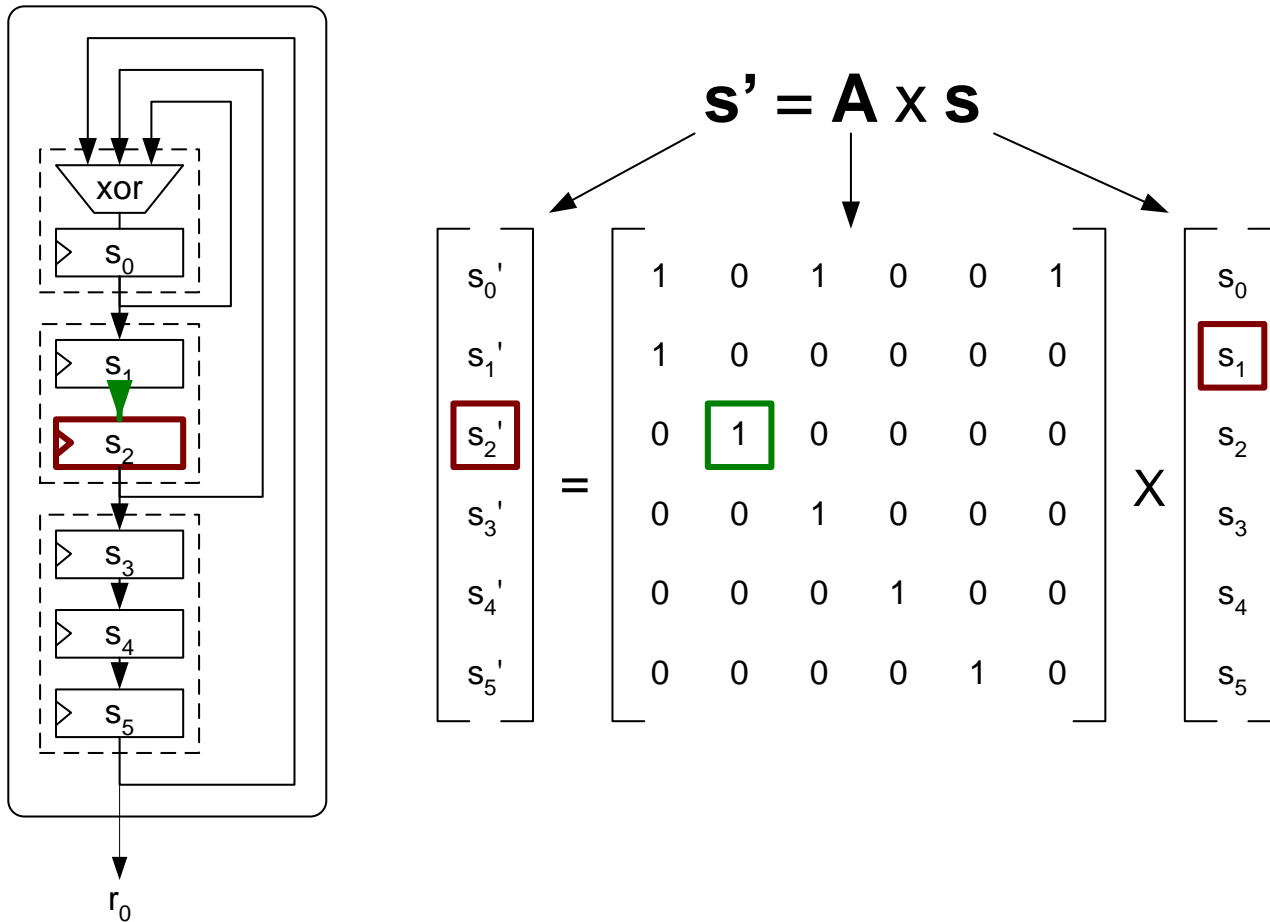

General Theory: Linear Recurrences

- The matrix \mathbf{A} defines a linear recurrence (mod-2)
 - Let \mathbf{s}_0 be the initial state of the LFSR
 - After one cycle: $\mathbf{s}_1 = \mathbf{A} \mathbf{s}_0$
 - After two cycles: $\mathbf{s}_2 = \mathbf{A} \mathbf{s}_1 = \mathbf{A} (\mathbf{A} \mathbf{s}_0) = \mathbf{A}^2 \mathbf{s}_0$
 - After i cycles: $\mathbf{s}_i = \mathbf{A}^i \mathbf{s}_0$
- Eventually the sequence must repeat (finite state)
 - For an n bit state the maximum possible period is $2^n - 1$
 - Can determine period by analysing \mathbf{A}
- Challenge: given requirements
 - Maximise period
 - Find best statistical quality subject to maximal period

LFSRs: Why are they so bad?

- Quality : have known statistical quality problems
- Period : LFSRs only make sense for $n < 128$
 - A period of $2^{128}-1$ is worryingly low for parallel simulations
 - Makes randomised seeding of parallel RNGs hazardous
- Efficiency : a 1-bit LFSR requires many resources
 - Needs four or five LUT-FF elements for each bit
- Scalability : the LFSR only provides one bit/cycle
 - Most applications need far more bits per cycle
 - Multiple bits requires independent parallel LFSRs
 - Parallel LFSRs = GFSR+XOR : **bad** reputation
- *Please don't use LFSRs for parallel Monte-Carlo...*


Previous FPGA RNGs: Software RNGs

- Take a software generator, implement in RTL
 - Popular choice: take advantage of existing algorithms
 - Mersenne Twister, SPRNG, lagged Fibonacci
- Software generators often not efficient in hardware
 - Use different operation costs: no bit-level ops or RAMs
 - Ignore data-dependencies; may not pipeline well
- Word-based generators provide 32 or 64-bit words
 - FPGA simulations often need 128+ random bits/cycle
 - Instantiating parallel generators is a poor solution
- Common practice: optimise SW algorithm for HW
 - But: linear recurrences have subtle properties
 - e.g. attempts to increase outputs/cycle -> unknown period


How can we create a *new* FPGA RNG

1. Define a general architecture for the generator
 - What sort of resources, and how are they connected?
 - What constraints are placed on the connections?
2. Create algorithm for constructing instances of RNG
 - Use random choices to make decisions about structure
3. Search for good instances of the generator
 - a. Generate a huge number of candidate RNG instances
 - b. Discard all candidates where constraints are not met
 - c. Extract matrix A for candidate RNGs
 - d. Discard RNGs which do not have maximum period
 - e. Select best remaining RNG according to quality metrics

Previous FPGA RNGs: LUT-Optimised

 

Improve Period: LUT-FIFO

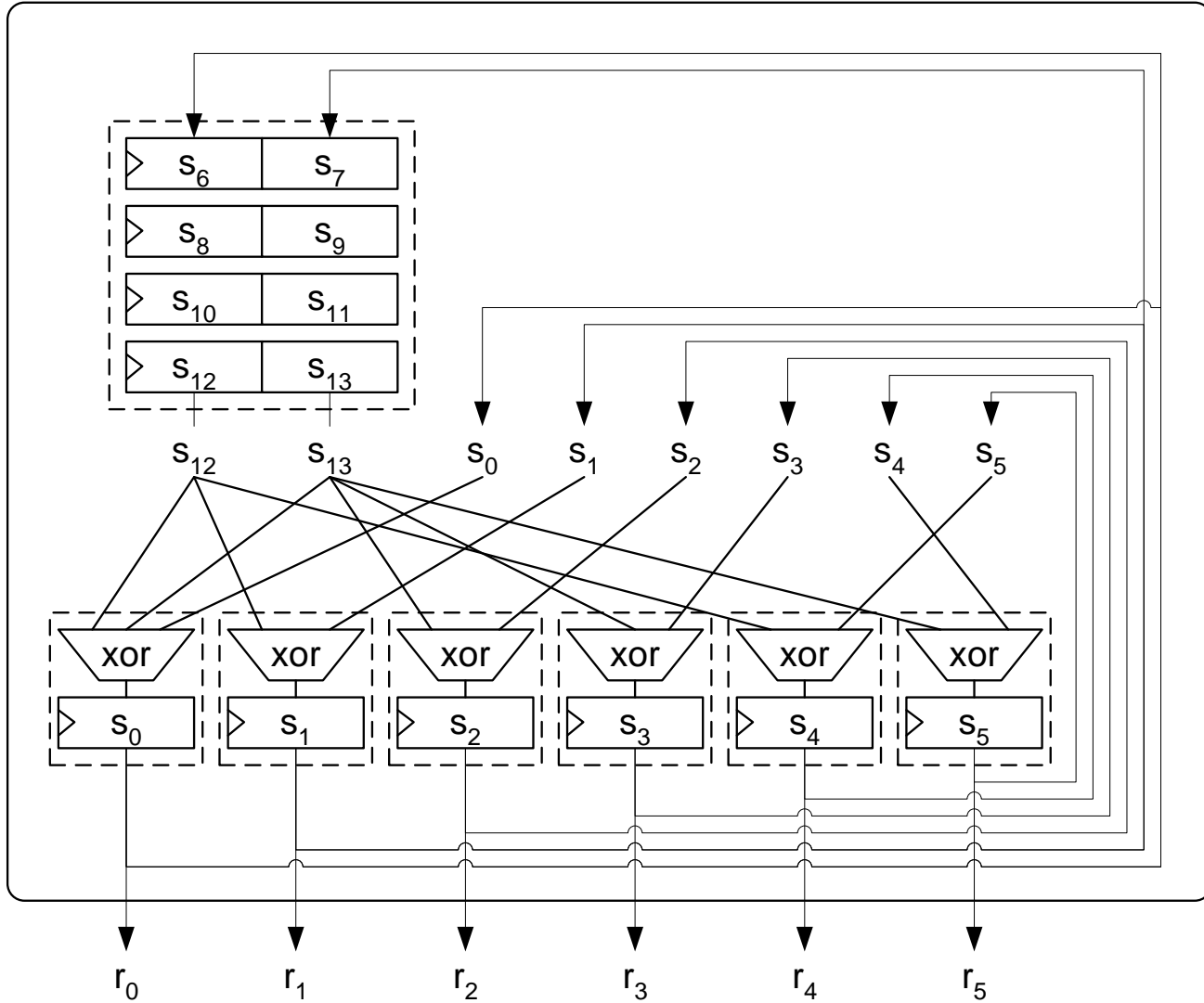


Why do we need *another* RNG?

- The LUT-Opt generator is very small and fast
 - Good as a building block for non-uniform generators
 - But: has some mild statistical problems
- The LUT-FIFO has superb quality and a huge period
 - Same class as Mersenne Twister, but more efficient
 - But: overkill for most applications, and requires block RAM
- Both generators are hard to distribute to users
 - Require carefully selected parameters
 - Impossible to include the code in papers
 - Full set of generators requires megabytes of VHDL

LUT-SR Generator: Goals

- Architecture - Efficient, Scalable, and Foolproof
 - Efficient : constant resources per generated bit
 - Scalable : quality and period scale with output width
 - Foolproof : no quality issues; appropriate for use anywhere
- Specification - Concise, Complete, and Open Source
 - Concise : generators described using a simple algorithm
 - Complete : **all** parameters and algorithms included in paper
 - Open Source : VHDL libraries made available online
- No excuses - if you're still using an LFSR... why?

The LUT-SR Architecture

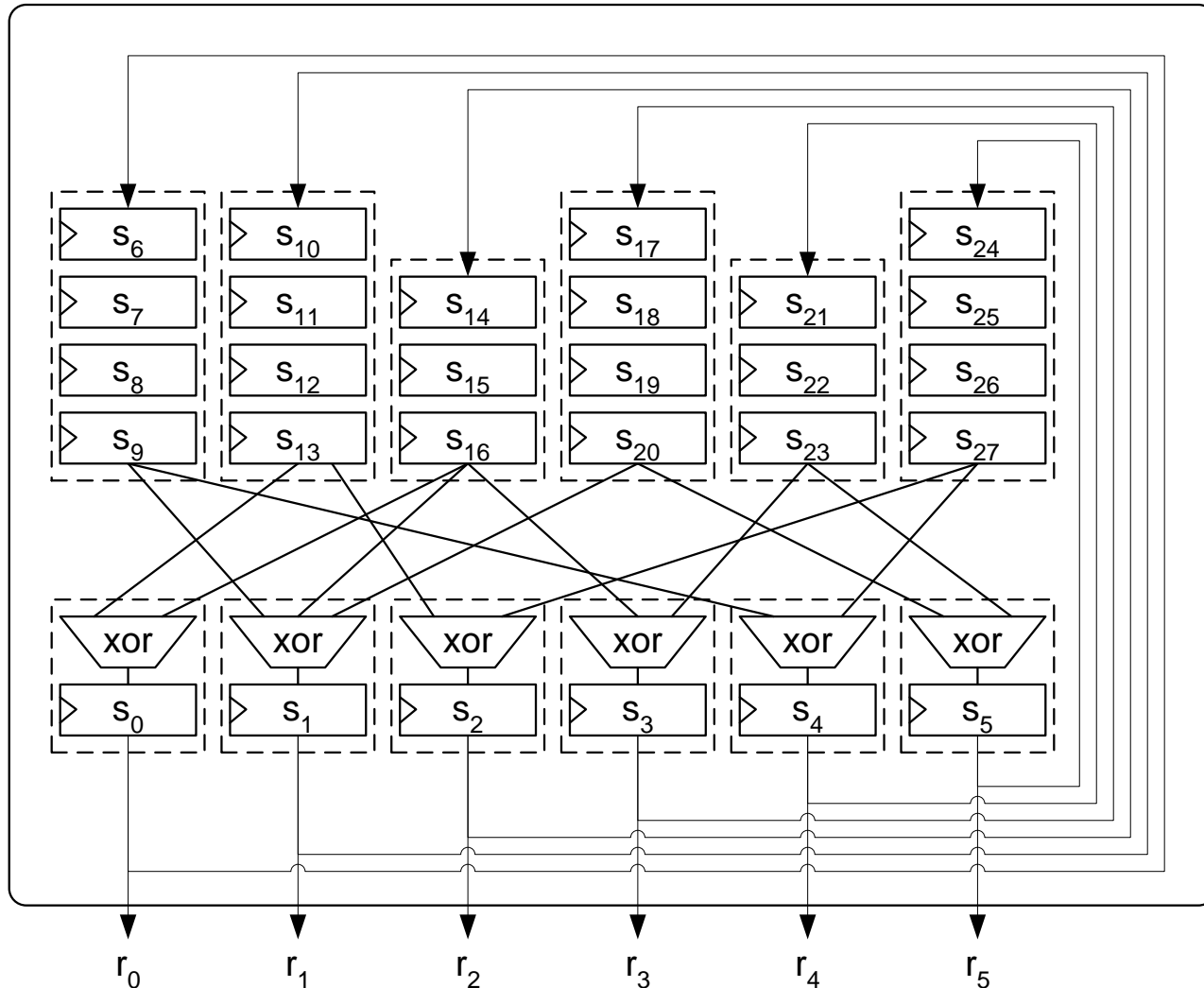


Architecture: Optimise Temporal Quality

- Outputs only depend on Shift-Register (SR) outputs
 - No direct dependency between previous and next output
 - Minimum dependency distance is depth of shortest SR
- Scale storage with output bits
 - Equidistribution - theoretical measure of auto-correlation
 - LUT-Opt: poor equidistribution due to 1:1 storage:output
 - LUT-FIFO: equidistribution decreases as outputs increase
 - LUT-SR: *equidistribution constant as output bits increase*
- Use Shift-Registers of different lengths
 - Increases mixing between bits in state
 - Improve “avalanche” property: time till one bit affects all bits


Initialisation: Managing RNG State

- Loading RNG state is important
 - We need to be able to put the RNG in a ***specific*** state
 - Parallel simulations have to manage RNG states carefully
 - Leapfrogging – single RNG sequence split among RNGs
 - Random initialisation – use random seed state for each RNG
- Loading RNG state is infrequent
 - 99.999% of the time is spent generating random bits
 - Can't spend lots of resources on initialisation
- Previous approaches tend to side-step initialisation
 - *Umm, including LUT-Opt and LUT-FIFO*
 - Suggested expensive parallel loading of state
- We can get initialisation for free, *if we are careful*


Initialisation: Finding a Cycle

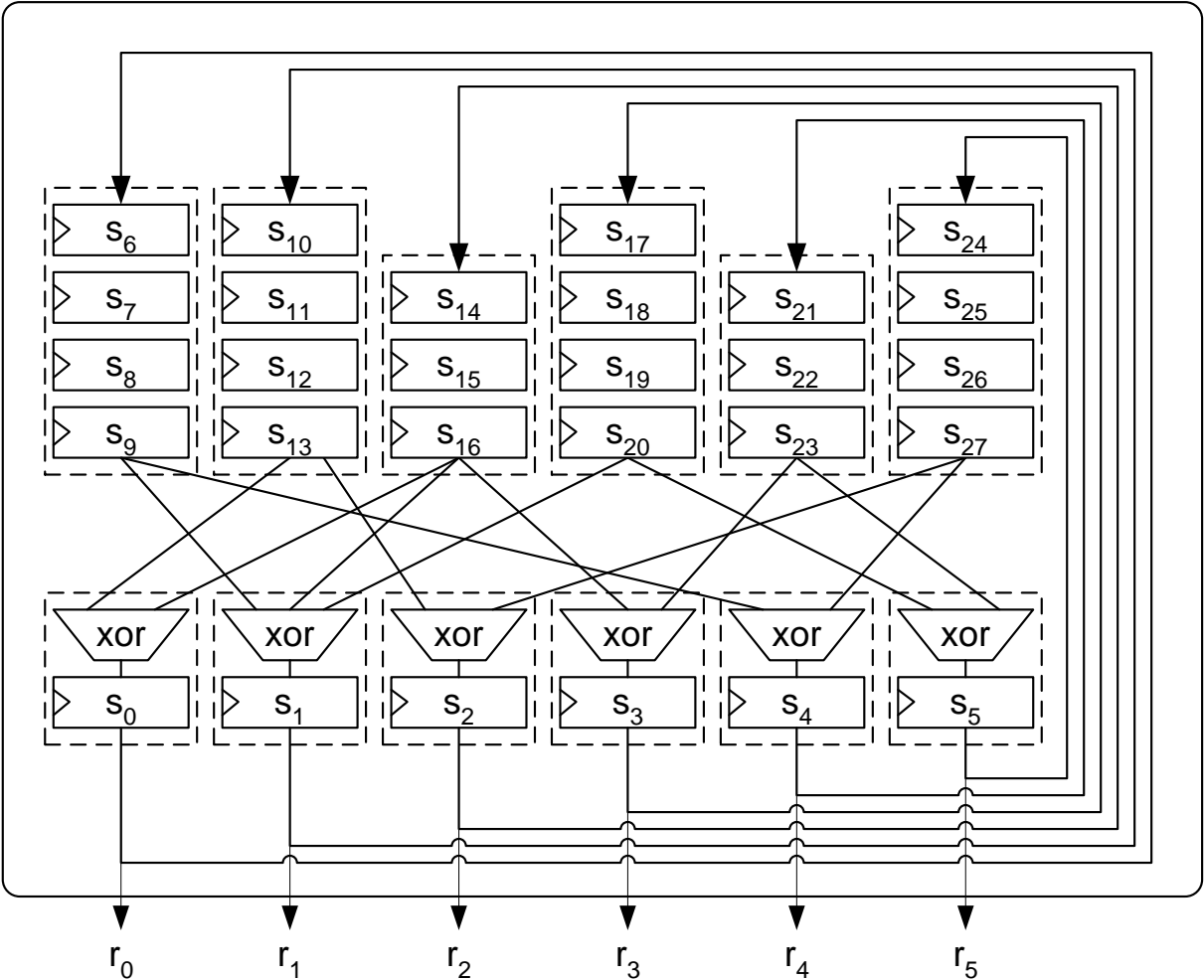


Initialisation: Finding a Cycle

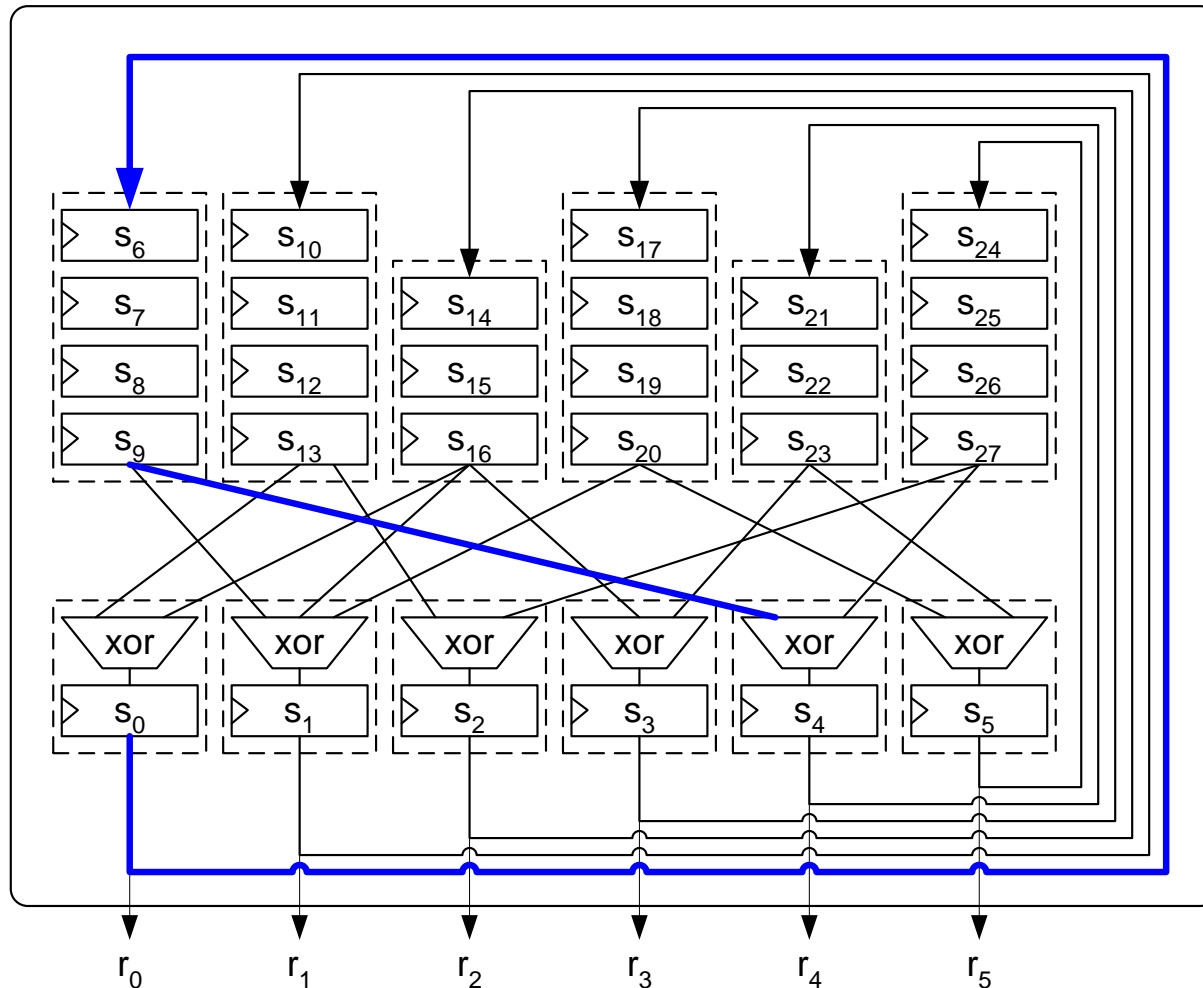


Initialisation: Finding a Cycle

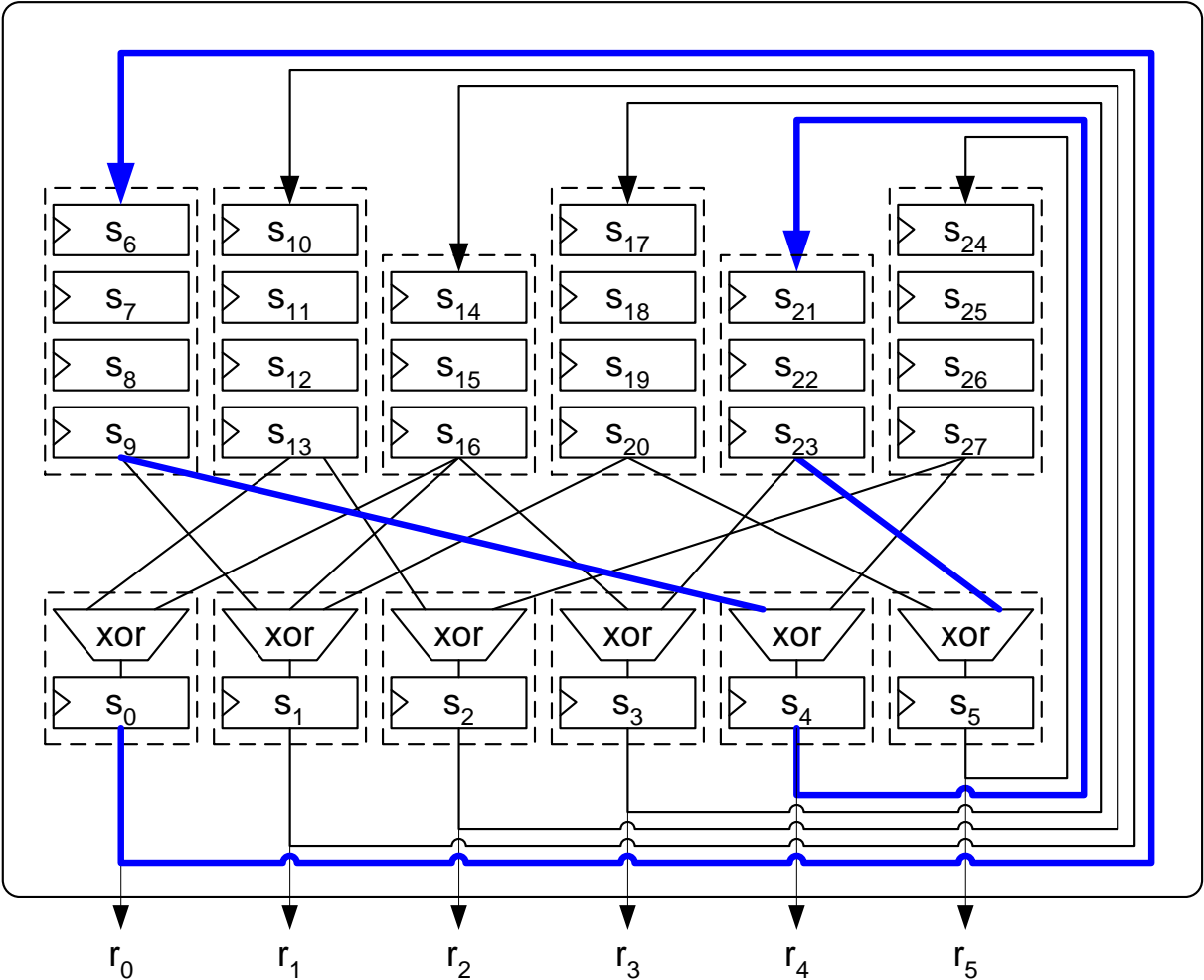


Initialisation: Finding a Cycle

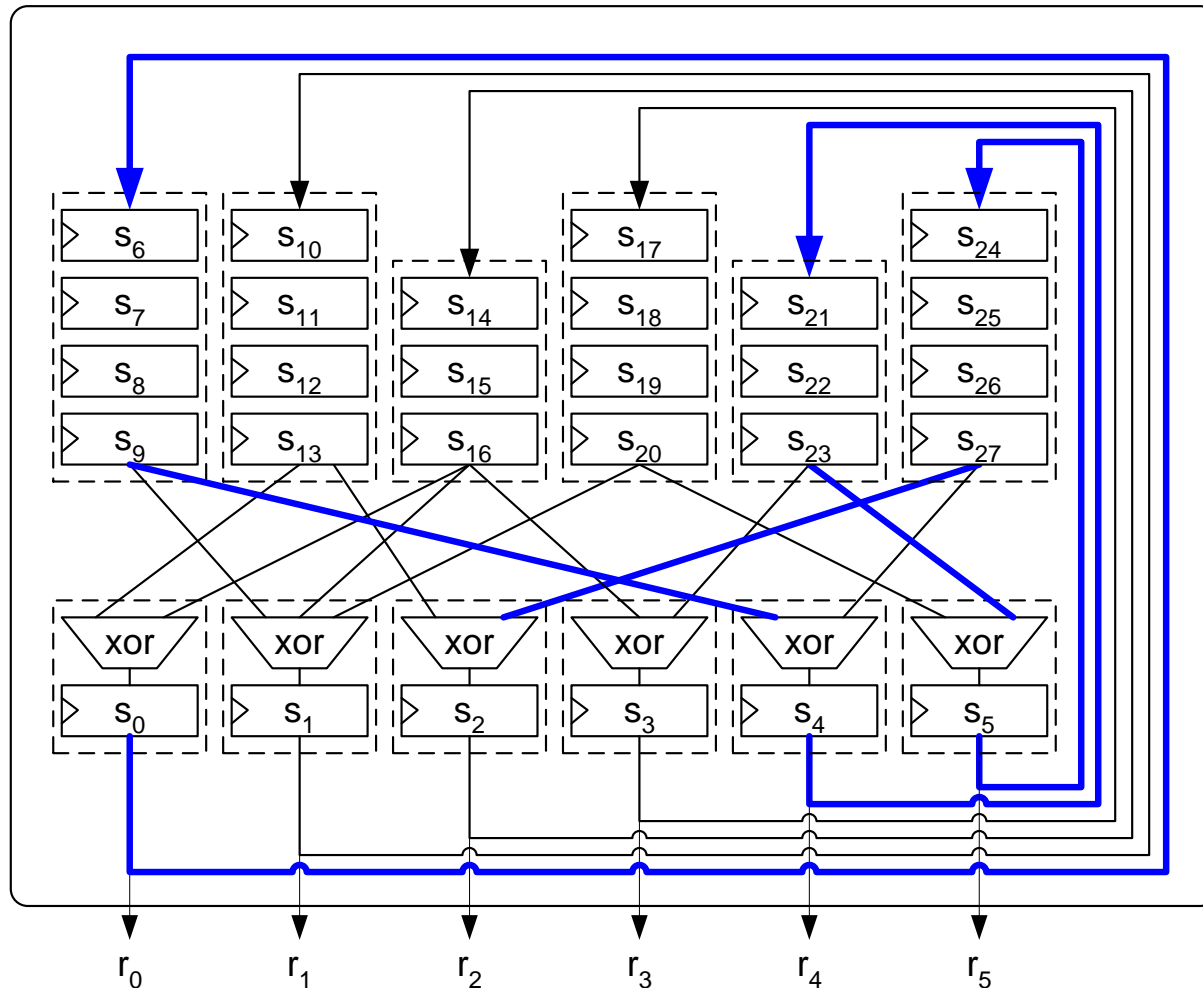


Initialisation: Finding a Cycle

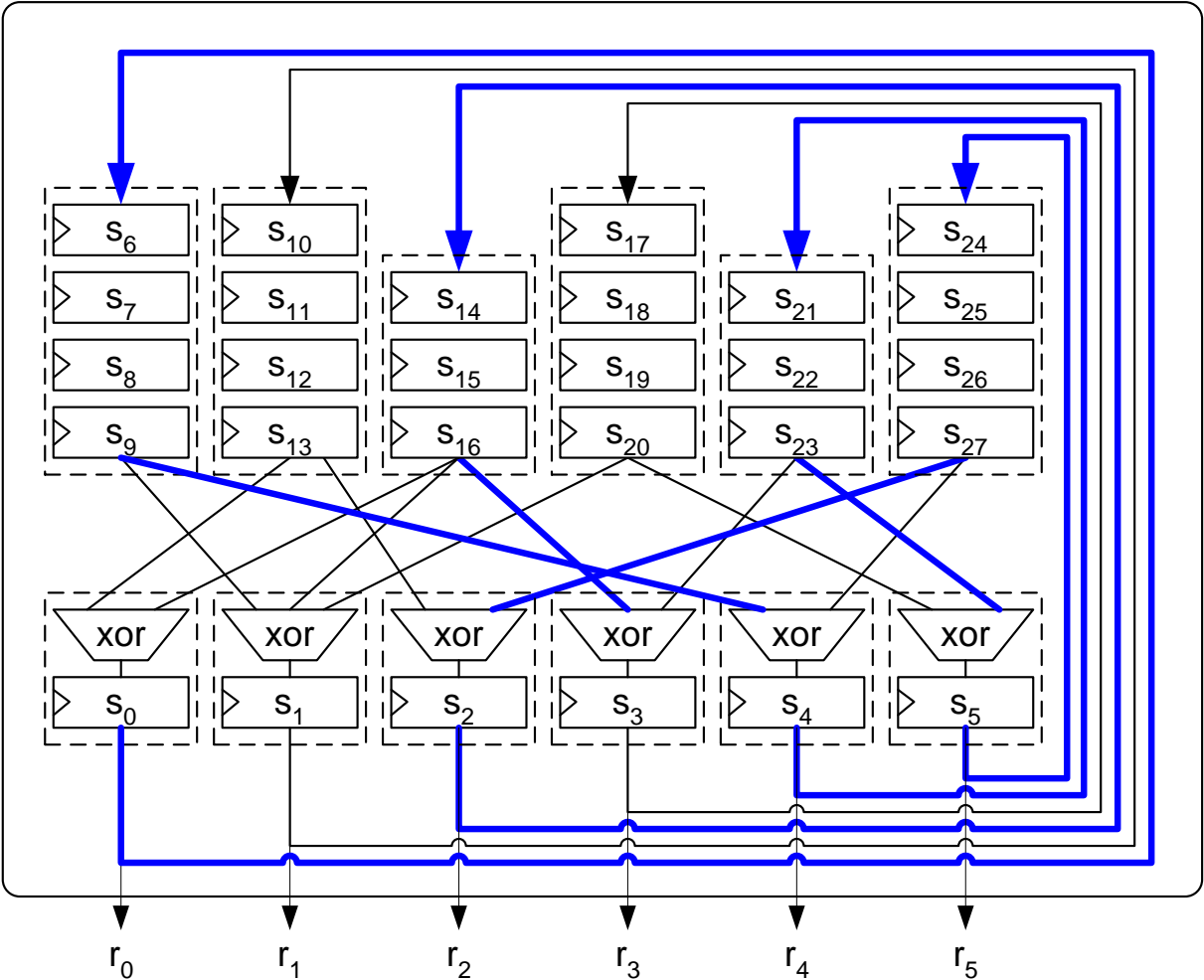


Initialisation: Finding a Cycle

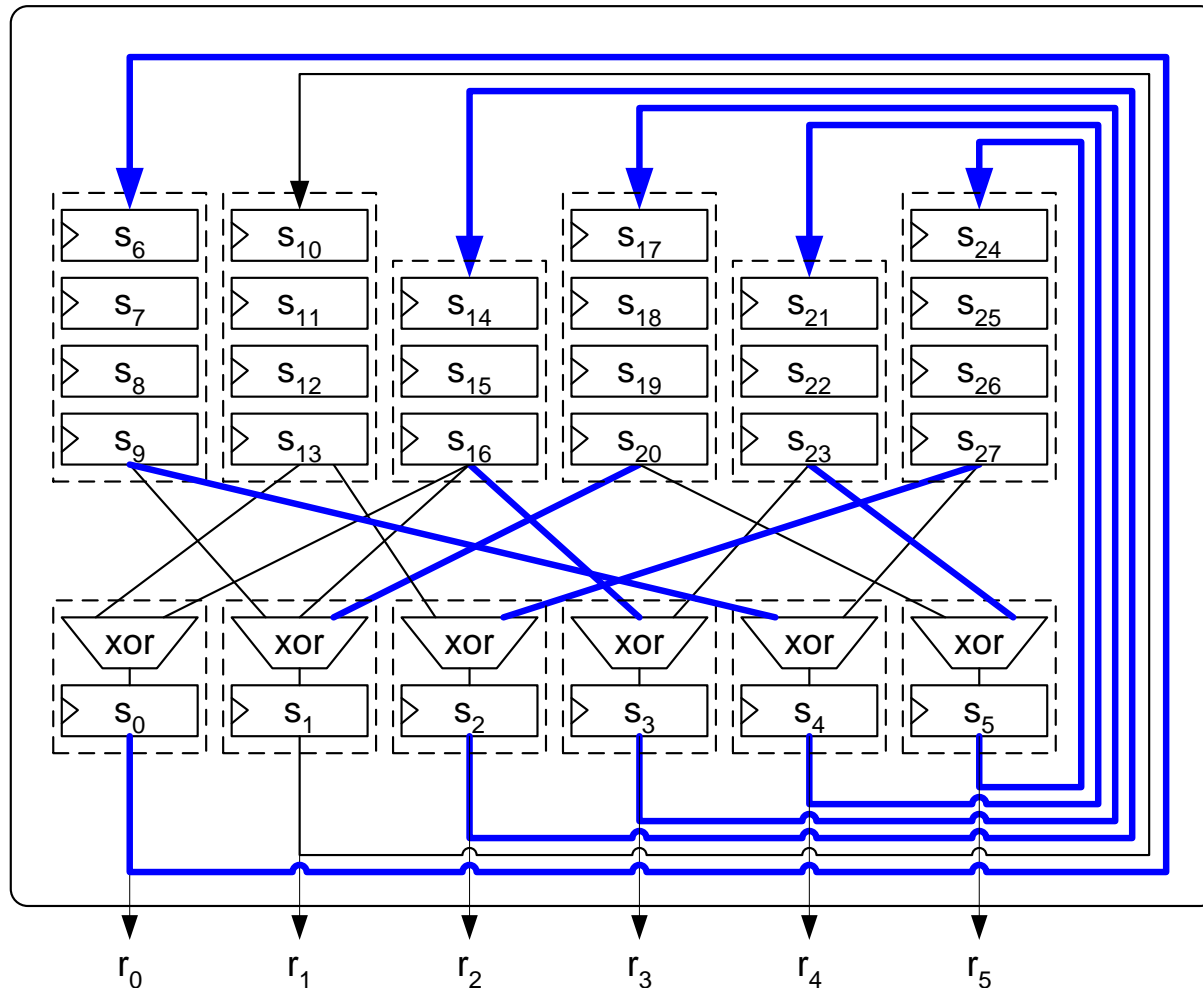

Initialisation: Finding a Cycle

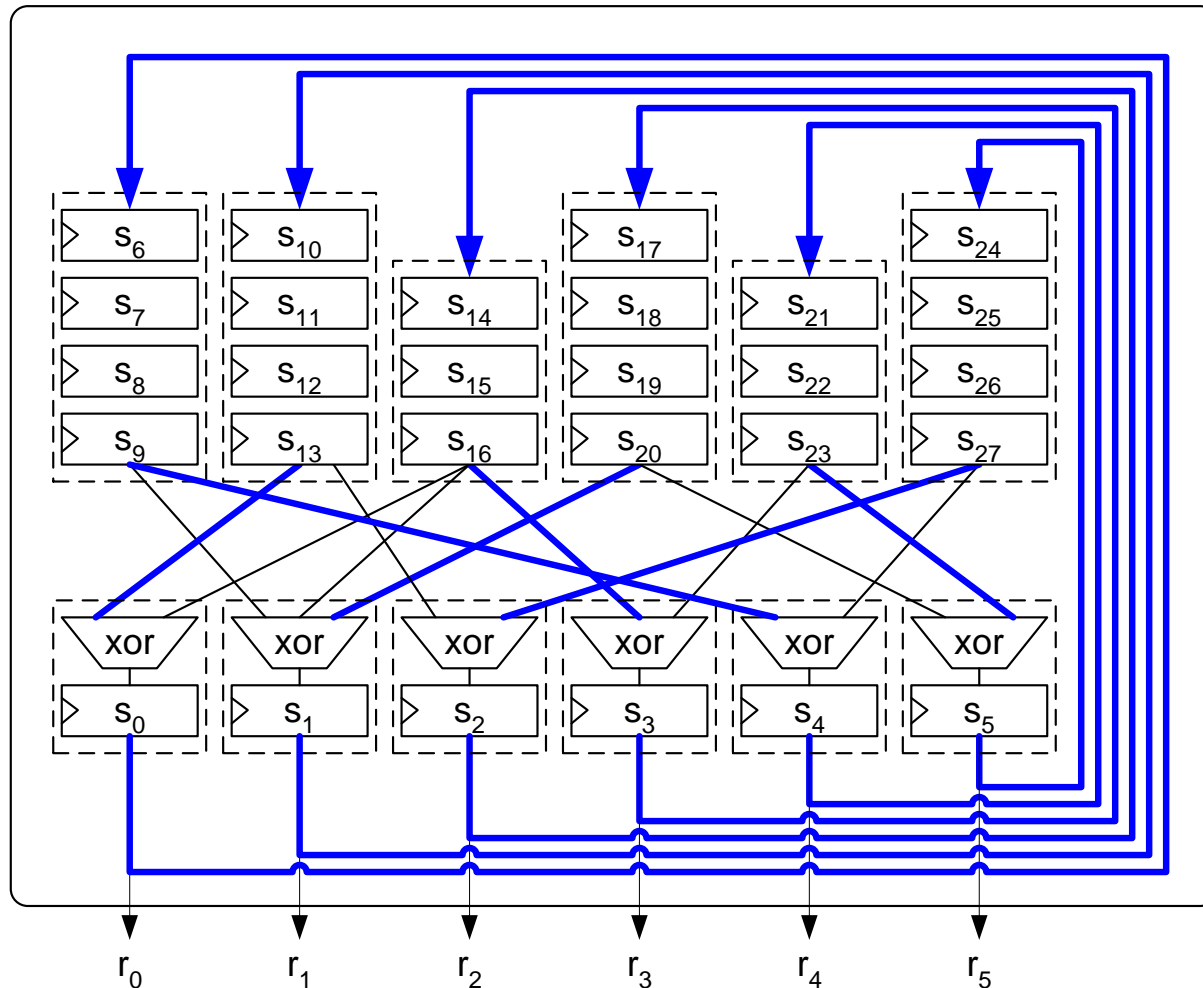

Initialisation: Opening Up the Cycle

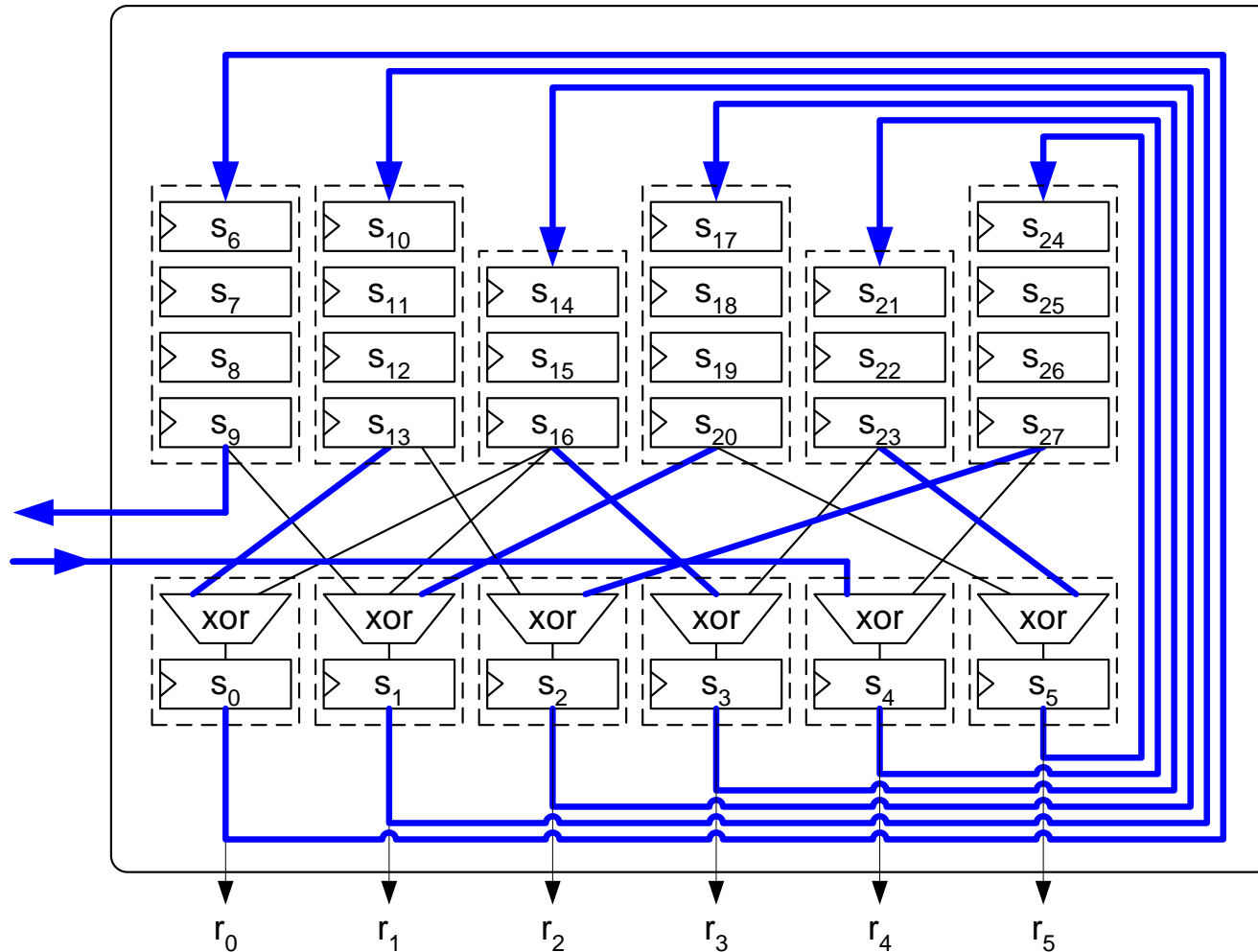

How do we find the cycle?

- Previous work casually suggested “just find a cycle”
 - **cough**, my paper on LUT-Opt generators
- Given an arbitrary generator, finding a cycle is slow
 - Well known graph problem: Hamiltonian cycle
 - Doesn't really work for large numbers of output bits
- Have to build the cycle into basic structure of RNG
 - **Start** with a cycle, then add extra taps on top

Specification of LUT-SR RNGs

- Four parameters describe type of RNG
 - n : Number of bits in the state
 - r : Number of output bits per cycle
 - t : Number of xor inputs per bit (e.g. for 6-LUT choose $t=5$)
 - k : Maximum shift register length (e.g. $k=32$ for SRL32)
- Each (n,r,t,k) describes a *huge* space
 - Many possible $n \times n$ **A** matrices matching our template
- We want to pick specific generators which:
 1. Match a specific parameterisation (n,r,t,k)
 2. Have the maximum possible period of 2^n-1
 3. Have excellent statistical properties


Specification of LUT-SR RNGs

- Describe LUT-SR RNGS using (n,r,t,k,s)
 - (n,r,t,k) describes the **class** of LUT-SR RNG
 - Free parameter s identifies an **instance** of the RNG class
- Provides a way to compactly describe RNGs
 - For example: $(n=1024,r=32,t=5,k=32,s=7240)$
 - Describes a LUT-SR generator with:
 - A period of $2^{1024}-1$, producing 32 random output bits per cycle
 - Designed for 5-input XOR gates and 32-bit shift registers
- Where does s come from?
 - Identifies the best instances, details in paper


Expand 5 parameters into RTL

1. Seed simple (software) RNG with free parameter s
2. Randomly extend FIFOs
 - While state bits of RNG is less than n
 - Choose a random output bit i in $[0, r)$
 - If $\text{fifo_length}(i) < k$ then extend $\text{fifo}(i)$
3. Create the shift permutation $i = i + 1 \pmod r$
 - This will form our loading cycle
4. Insert XOR connections
 - For i in $[1, t)$
 1. Create a random permutation of $[0, r) \rightarrow [0, r)$
 2. Add permutation as XOR connections
5. Permute the output bits

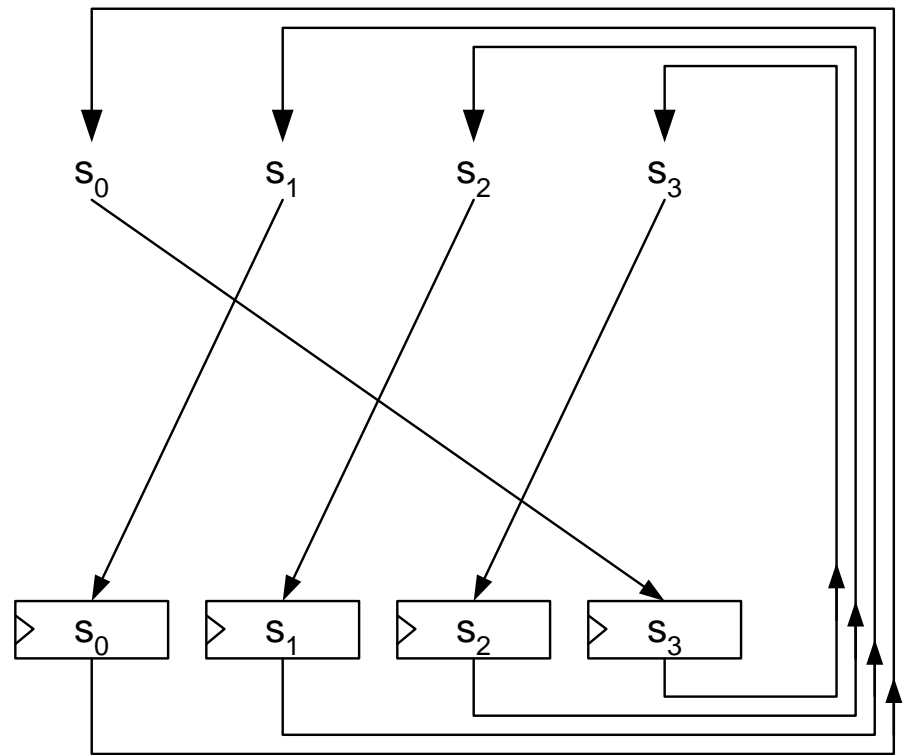
1. Initialise RNG using s
2. Create shift cycle



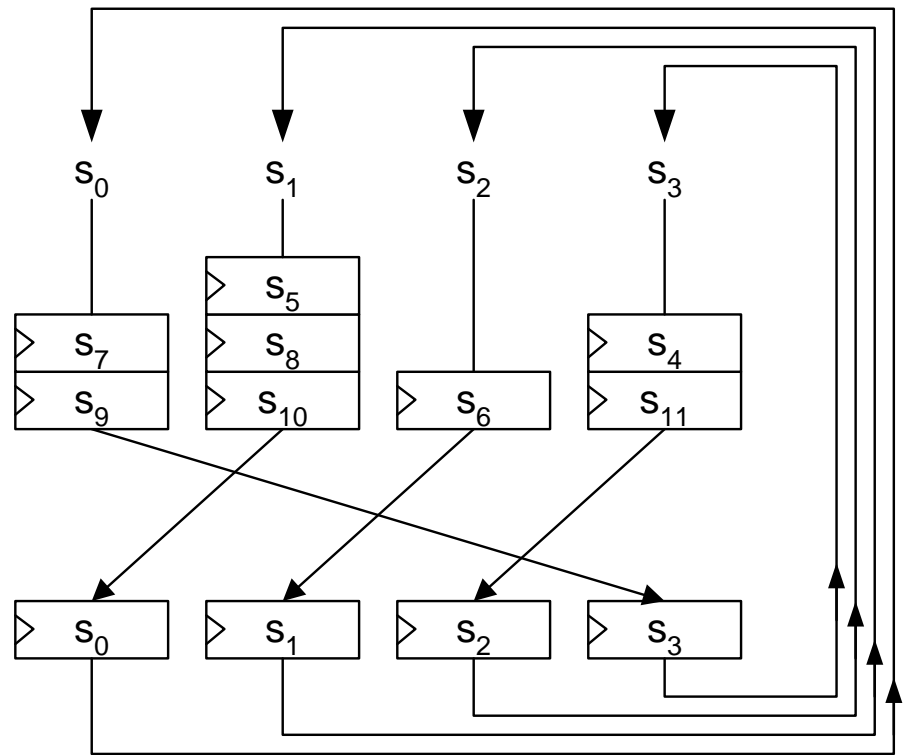
1. Initialise RNG using s
2. Create shift cycle
3. Randomly extend FIFOs



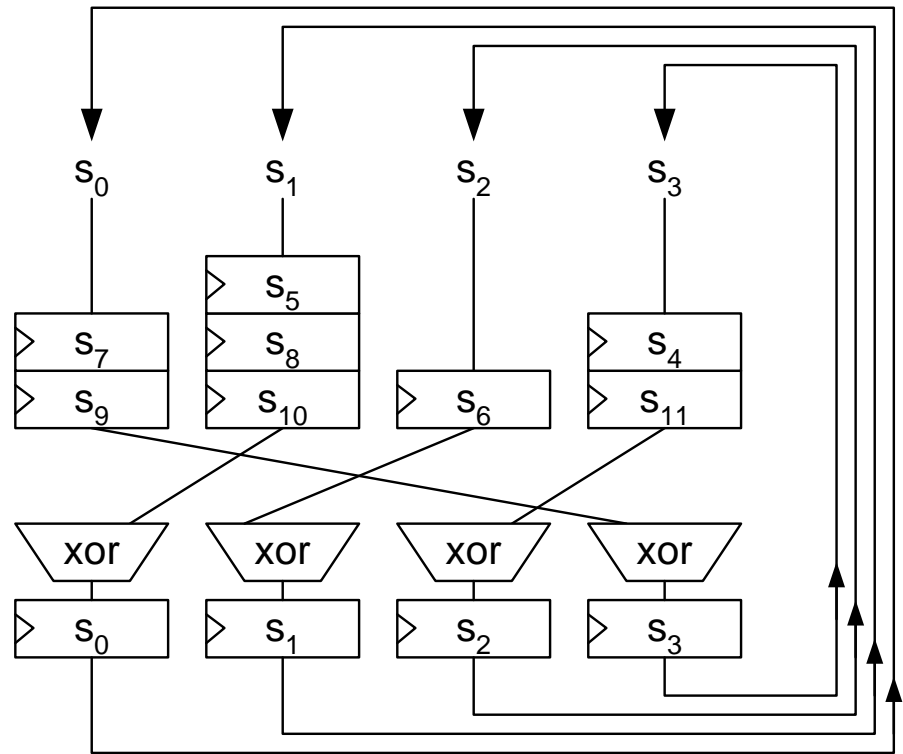
1. Initialise RNG using s
2. Create shift cycle
3. Randomly extend FIFOs
4. Build XOR connections



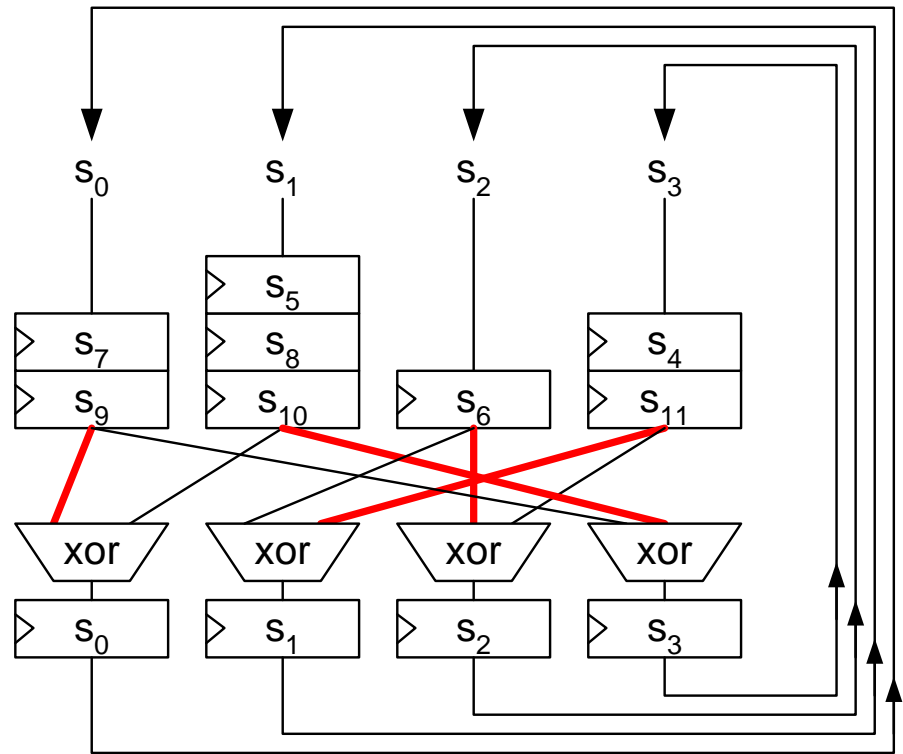
1. Initialise RNG using s
2. Create shift cycle
3. Randomly extend FIFOs
4. Build XOR connections
 - Random permutations



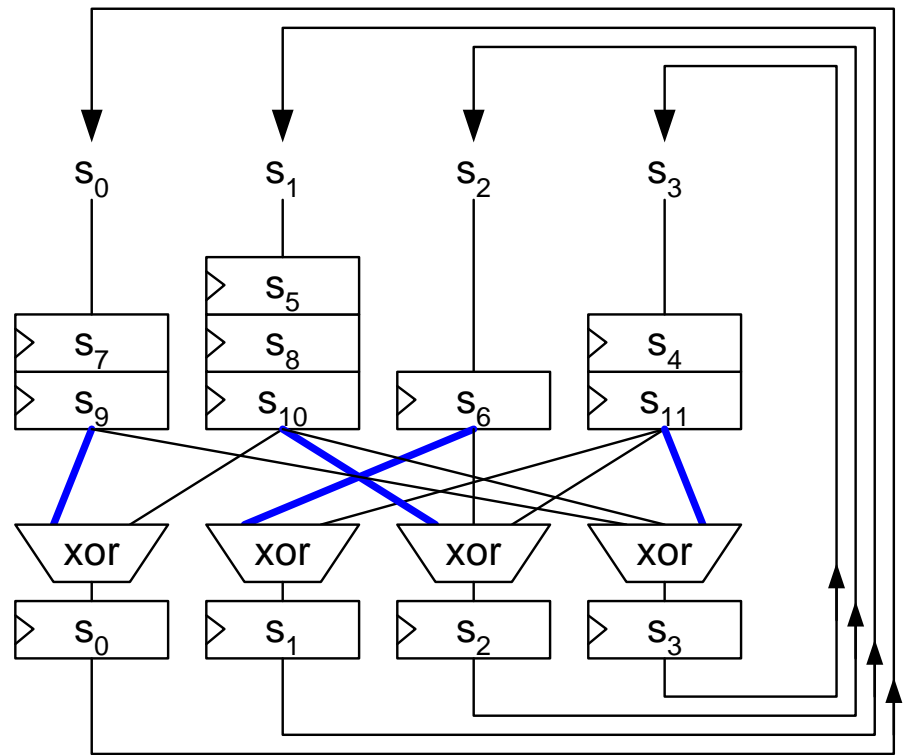
1. Initialise RNG using s
2. Create shift cycle
3. Randomly extend FIFOs
4. Build XOR connections
 - Random permutations
 - Keep existing edges



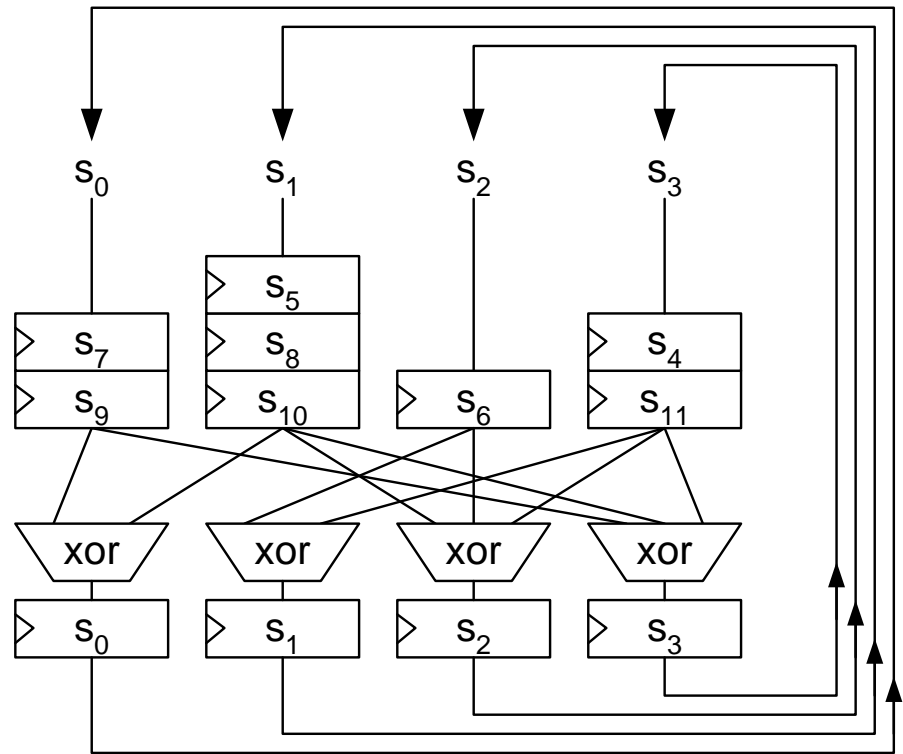1. Initialise RNG using s
2. Create shift cycle
3. Randomly extend FIFOs
4. Build XOR connections
 - Random permutations
 - Keep existing edges



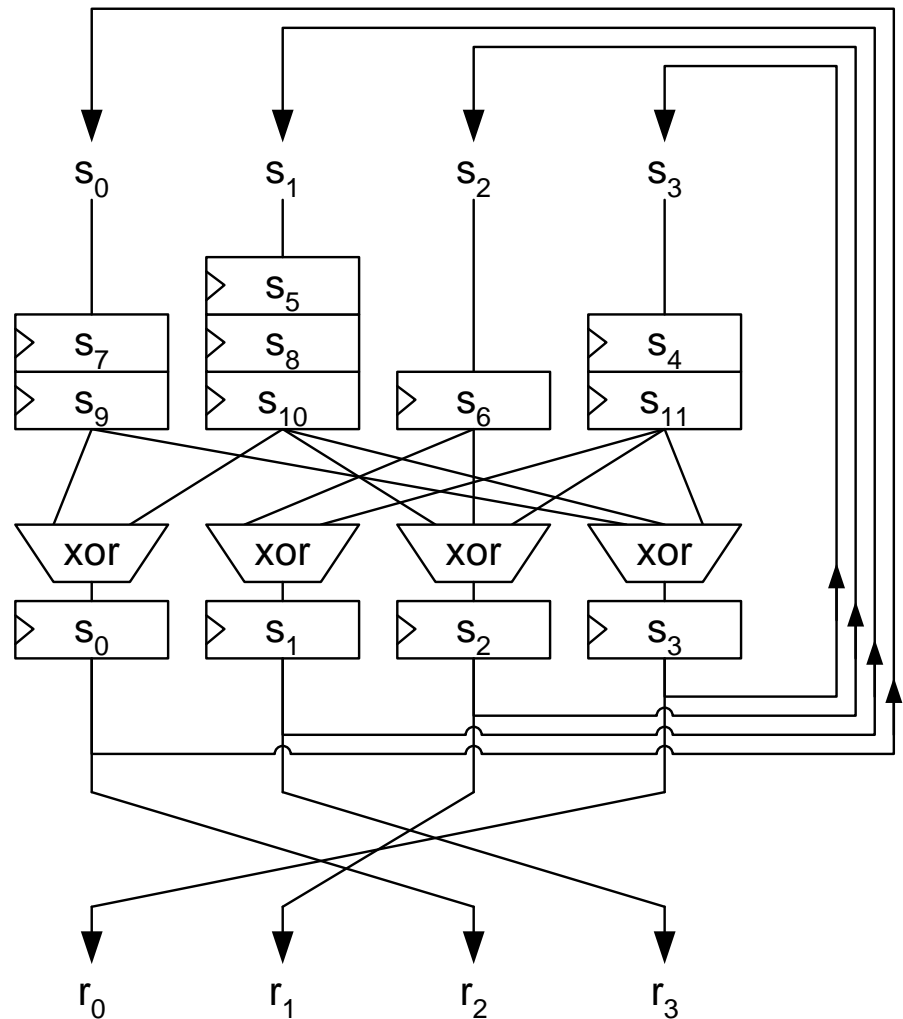1. Initialise RNG using s
2. Create shift cycle
3. Randomly extend FIFOs
 - Random permutations
 - Keep existing edges
5. Permute output bits



Why write the algorithm this way?

- Not the most efficient algorithm for ***finding*** RNGs
 - Could modify chances of each s giving a valid RNG
 - Algorithm is quite slow when building up FIFOs
- But very efficient algorithm for ***instantiating*** RNGs
 - Code is very small and easy to understand
 - Self-contained and can be copied and pasted
- Algorithm design and spec. is biased towards users
 - There are many potential users (instantiators) of RNGs
 - There is only one person, me, doing the searching

Complete specification in the paper

- Provide everything in one column of C++
 1. Expansion algorithm: convert 5-tuple into RNG
 2. Pseudo-RTL source-code printer
 - Dump the RNG in a form that can be turned into VHDL or C
 - Sigh, or Verilog if you hate type-safety *that* much...
 3. Bit-accurate software simulator
- Paper includes tuples for a variety of r and t
 - Hopefully covers useful spectrum for most people
- Plus: online open-source repository
 - Generator for VHDL RNGs and test-benches
 - http://www.doc.ic.ac.uk/~dt10/research/rngs-fpga-lut_sr.html
 - Or try googling “LUT-SR RNG”, or look in paper for the URL

Comparison with other RNGs

	n	r	Quality	RAM	LUT	FF	r/LUT
Tauss113	113	32	Medium	0	87	208	0.37
MT19937	19937	32	Good	2	278	?	0.12
LFSR-160	160	32	Poor	0	448	384	0.07
LUT-OPT	512	512	Medium	0	513	512	1.00
LUT-FIFO	11213	89	Good	1	115	181	0.77
LUT-SR	1024	32	Good	0	64	64	0.50

Conclusion

- New approach for producing optimised RNG
 - Linear recurrence theory: ensure statistical quality
 - Compact RNG description using 5 parameters
- The LUT-SR generator is optimised for FPGAs
 - Bit-wise LUTs to improve mixing within state
 - Bit-wise SRs to increase period using cheap storage
- Provides a good balance between quality and area
 - High performance, only two LUTs per random bit
 - Provides long periods and great statistical quality
- Easy to use: VHDL available, or use the paper spec.
 - Friends don't let friends use LFSRs...