

Pipelined FPGA Adders

Bogdan Pasca

joint work with:

Florent de Dinechin and **Hong Diep Nguyen**

FPL, Aug. 31st - Sep. 2nd, 2010



Why a paper on integer addition on FPGAs in 2010?

Why a paper on integer addition on FPGAs in 2010?

The FloPoCo project

The FloPoCo project

- Goals
 - provide new and exotic arithmetic operators
 - ▶ highly complex operators (floating-point elementary functions)
 - ▶ specialized operators (constant multipliers, squarers)

The FloPoCo project

- Goals
 - provide new and exotic arithmetic operators
 - ▶ highly complex operators (floating-point elementary functions)
 - ▶ specialized operators (constant multipliers, squarers)
 - ▶ ... (currently about ∞ operators in about 50 classes)

Why a paper on integer addition on FPGAs in 2010?

The FloPoCo project

- Goals
 - provide new and exotic arithmetic operators
 - ▶ highly complex operators (floating-point elementary functions)
 - ▶ specialized operators (constant multipliers, squarers)
 - ▶ ... (currently about ∞ operators in about 50 classes)
 - optimized for a wide range of contexts
 - ▶ adapt to the application's precision needs
 - ▶ match target hardware
 - ▶ run at target frequency
 - ▶ minimize resource consumption

Why a paper on integer addition on FPGAs in 2010?

The FloPoCo project

- Goals
 - provide new and exotic arithmetic operators
 - ▶ highly complex operators (floating-point elementary functions)
 - ▶ specialized operators (constant multipliers, squarers)
 - ▶ ... (currently about ∞ operators in about 50 classes)
 - optimized for a wide range of contexts
 - ▶ adapt to the application's precision needs
 - ▶ match target hardware
 - ▶ run at target frequency
 - ▶ minimize resource consumption
 - in an easy to use open-source framework.

Why a paper on integer addition on FPGAs in 2010?

The FloPoCo project

- Goals
 - provide new and exotic arithmetic operators
 - ▶ highly complex operators (floating-point elementary functions)
 - ▶ specialized operators (constant multipliers, squarers)
 - ▶ ... (currently about ∞ operators in about 50 classes)
 - optimized for a wide range of contexts
 - ▶ adapt to the application's precision needs
 - ▶ match target hardware
 - ▶ run at target frequency
 - ▶ minimize resource consumption
 - in an easy to use open-source framework.
- Method:
 - assemble sub-components built for the same target frequency

Why a paper on integer addition on FPGAs in 2010?

The FloPoCo project

- Goals
 - provide new and exotic arithmetic operators
 - ▶ highly complex operators (floating-point elementary functions)
 - ▶ specialized operators (constant multipliers, squarers)
 - ▶ ... (currently about ∞ operators in about 50 classes)
 - optimized for a wide range of contexts
 - ▶ adapt to the application's precision needs
 - ▶ match target hardware
 - ▶ run at target frequency
 - ▶ minimize resource consumption
 - in an easy to use open-source framework.
- Method:
 - assemble sub-components built for the same target frequency

Addition is the most useful of these components

```
(...)  
| | | | | |---Entity IntAdder_16_f325_slice_SRL_noBUFFER_uid10_Alternative:  
| | | | | | Not pipelined  
(...)  
| | | | | |---Entity IntAdder_52_f400_slice_SRL_noBUFFER_uid16_Classical:  
| | | | | | Pipeline depth = 1  
| | | | | |---Entity IntCompressorTree_52_2_uid15:  
| | | | | | Pipeline depth = 1  
| | | | | |---Entity IntTruncMultiplier_30_34_35_signed:  
| | | | | | Pipeline depth = 4  
| | | | | |---Entity IntAdder_42_f400_slice_SRL_BUFFER_uid17_Classical:  
| | | | | | Pipeline depth = 1  
| | | | | |---Entity PolynomialEvaluator_d2:  
| | | | | | Pipeline depth = 15  
|---Entity FunctionEvaluator:  
| Pipeline depth = 17  
|---Entity IntAdder_48_f400_slice_SRL_noBUFFER_uid18_Classical:  
| Pipeline depth = 2  
|---Entity IntAdder_48_f400_slice_SRL_noBUFFER_uid19_Classical:  
| Pipeline depth = 2  
| | |---Entity IntAdder_85_f325_slice_SRL_noBUFFER_uid22_Classical:  
| | | Pipeline depth = 1  
| | |---Entity IntCompressorTree_85_3_uid21:  
| | | Pipeline depth = 2  
|---Entity IntMultiplier_47_48_uid20:  
| Pipeline depth = 6  
|---Entity IntAdder_57_f400_slice_SRL_noBUFFER_uid23_Classical:  
| Pipeline depth = 2  
|---Entity IntAdder_65_f400_slice_SRL_noBUFFER_uid24_Classical:  
| Pipeline depth = 2  
Entity FPEXP_11.52.400:  
Pipeline depth = 52
```

```
(...)  
| | | | |---Entity IntAdder_16_f325_slice_SRL_noBUFFER_uid10_Alternative:  
| | | | | Not pipelined  
(...)  
| | | | |---Entity IntAdder_52_f400_slice_SRL_noBUFFER_uid16_Classical:  
| | | | | Pipeline depth = 1  
| | | | |---Entity IntCompressorTree_52_2_uid15:  
| | | | | Pipeline depth = 1  
| | |---Entity IntTruncMultiplier_30_34_35_signed:  
| | | Pipeline depth = 4  
| | |---Entity IntAdder_42_f400_slice_SRL_BUFFER_uid17_Classical:  
| | | Pipeline depth = 1  
| |---Entity PolynomialEvaluator_d2:  
| | Pipeline depth = 15  
|---Entity FunctionEvaluator:  
| Pipeline depth = 17  
|---Entity IntAdder_48_f400_slice_SRL_noBUFFER_uid18_Classical:  
| Pipeline depth = 2  
|---Entity IntAdder_48_f400_slice_SRL_noBUFFER_uid19_Classical:  
| Pipeline depth = 2  
| | |---Entity IntAdder_85_f325_slice_SRL_noBUFFER_uid22_Classical:  
| | | Pipeline depth = 1  
| | |---Entity IntCompressorTree_85_3_uid21:  
| | | Pipeline depth = 2  
|---Entity IntMultiplier_47_48_uid20:  
| Pipeline depth = 6  
|---Entity IntAdder_57_f400_slice_SRL_noBUFFER_uid23_Classical:  
| Pipeline depth = 2  
|---Entity IntAdder_65_f400_slice_SRL_noBUFFER_uid24_Classical:  
| Pipeline depth = 2  
Entity FPEXP_11.52.400:  
Pipeline depth = 52
```

flopoco -frequency=400 FPEXP 11 52


(double precision)

```
(...)  
| | | | |---Entity IntAdder_16_f325_slice_SRL_noBUFFER_uid10_Alternative:  
| | | | | Not pipelined  
(...)  
| | | | |---Entity IntAdder_52_f400_slice_SRL_noBUFFER_uid16_Classical:  
| | | | | Pipeline depth = 1  
| | | | |---Entity IntCompressorTree_52_2_uid15:  
| | | | | Pipeline depth = 1  
| | |---Entity IntTruncMultiplier_30_34_35_signed:  
| | | Pipeline depth = 4  
| | |---Entity IntAdder_42_f400_slice_SRL_BUFFER_uid17_Classical:  
| | | Pipeline depth = 1  
| |---Entity PolynomialEvaluator_d2:  
| | Pipeline depth = 15  
|---Entity FunctionEvaluator:  
| Pipeline depth = 17  
|---Entity IntAdder_48_f400_slice_SRL_noBUFFER_uid18_Classical:  
| Pipeline depth = 2  
|---Entity IntAdder_48_f400_slice_SRL_noBUFFER_uid19_Classical:  
| Pipeline depth = 2  
| | |---Entity IntAdder_85_f325_slice_SRL_noBUFFER_uid22_Classical:  
| | | Pipeline depth = 1  
| | |---Entity IntCompressorTree_85_3_uid21:  
| | | Pipeline depth = 2  
|---Entity IntMultiplier_47_48_uid20:  
| Pipeline depth = 6  
|---Entity IntAdder_57_f400_slice_SRL_noBUFFER_uid23_Classical:  
| Pipeline depth = 2  
|---Entity IntAdder_65_f400_slice_SRL_noBUFFER_uid24_Classical:  
| Pipeline depth = 2  
Entity FPEXP_11.52.400:  
Pipeline depth = 52
```

```
(...)  
| | | | | |---Entity IntAdder_16_f200_slice_SRL_noBUFFER_uid10_Alternative:  
| | | | | | Not pipelined  
(...)  
| | | | | |---Entity IntAdder_52_f200_slice_SRL_noBUFFER_uid16_Alternative:  
| | | | | | Not pipelined  
| | | | | |---Entity IntCompressorTree_52_2_uid15:  
| | | | | | Not pipelined  
| | |---Entity IntTruncMultiplier_30_34_35_signed:  
| | | Pipeline depth = 2  
| | |---Entity IntAdder_42_f200_slice_SRL_BUFFER_uid17_Classical:  
| | | Not pipelined  
| |---Entity PolynomialEvaluator_d2:  
| | Pipeline depth = 7  
|---Entity FunctionEvaluator:  
| Pipeline depth = 9  
|---Entity IntAdder_48_f200_slice_SRL_noBUFFER_uid18_Alternative:  
| Pipeline depth = 1  
|---Entity IntAdder_48_f200_slice_SRL_noBUFFER_uid19_Alternative:  
| Pipeline depth = 1  
| | |---Entity IntAdder_85_f200_slice_SRL_noBUFFER_uid22_Alternative:  
| | | Pipeline depth = 1  
| | |---Entity IntCompressorTree_85_3_uid21:  
| | | Pipeline depth = 1  
|---Entity IntMultiplier_47_48_uid20:  
| Pipeline depth = 5  
|---Entity IntAdder_57_f200_slice_SRL_noBUFFER_uid23_Alternative:  
| Pipeline depth = 1  
|---Entity IntAdder_65_f200_slice_SRL_noBUFFER_uid24_Alternative:  
| Pipeline depth = 1  
Entity FPExp_11.52_200:  
Pipeline depth = 23
```


This article

 How to generate "best" **addition operator** from user **specifications**



This article

 
How to generate "best" **addition operator** from user **specifications**



- elementary block resource estimation
- selection among possible implementations


What?
 
```
signal R, X, Y: std_logic_vector(w-1 downto 0);  
signal Cin: std_logic;  
begin  
  ...  
  R <= X + Y + Cin;  
  ...  
end architecture;
```




What?
 
```
signal R, X, Y: std_logic_vector(w-1 downto 0);  
signal Cin: std_logic;  
begin  
  ...  
  l: fast_but_large_adder port map(X, Y, Cin, R); --pipeline depth=0  
  ...  
end architecture;
```



What?
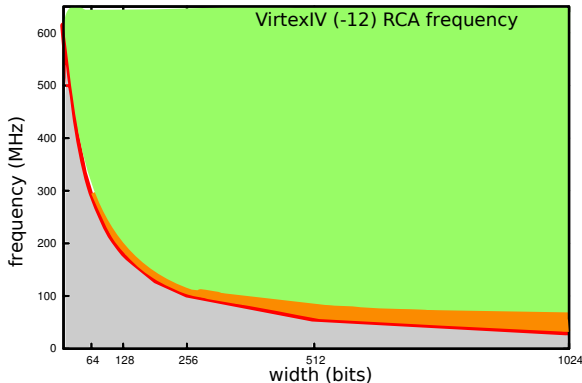
```
signal R, X, Y: std_logic_vector(w-1 downto 0);  
signal Cin: std_logic;  
begin  
  ...  
  l: fast_pipelined_adder port map(X, Y, Cin, R); --pipeline depth=X  
  ...  
end architecture;
```



Literature

- large number of VLSI studies [Mul89, EL04, DP96, US93]
Q: Why not reuse them?

Literature

- large number of VLSI studies [Mul89, EL04, DP96, US93]

Q: Why not reuse them?

- most hypotheses **false** for FPGA
- new architecture → **new rules**
- some ideas can still be recycled

Literature

- large number of VLSI studies [Mul89, EL04, DP96, US93]
Q: Why not reuse them?
 - most hypotheses **false** for FPGA
 - new architecture → **new rules**
 - some ideas can still be recycled
- Q: What about FPGA literature?
 - [XY98]: low-latency **unpipelined** adders
 - [MJE97]: Compression tree using a (naive) final pipelined adder
 - Other more recent papers on accumulation or compression trees

[XY98] Shanzhen Xing and William W.h. Yu.
FPGA Adders: Performance Evaluation and Optimal Design.

[MJE97] Peiro Marcos Martinez, Valls Javier, and Boemo Eduardo.
On the design of FPGA-based Multioperand Pipeline Adders.

Literature


- large number of VLSI studies [Mul89, EL04, DP96, US93]
Q: Why not reuse them?
 - most hypotheses **false** for FPGA
 - new architecture → **new rules**
 - some ideas can still be recycled
- Q: What about FPGA literature?
 - [XY98]: low-latency **unpipelined** adders
 - [MJE97]: Compression tree using a (naive) final pipelined adder
 - Other more recent papers on accumulation or compression trees

But no comprehensive study on **pipelined FPGA addition**

-
- [XY98] [Shanzhen Xing and William W.h. Yu.](#)
FPGA Adders: Performance Evaluation and Optimal Design.
- [MJE97] [Peiro Marcos Martinez, Valls Javier, and Boemo Eduardo.](#)
On the design of FPGA-based Multioperand Pipeline Adders.

Ripple-Carry-Adder

 
```
signal R, X, Y: std_logic_vector(w-1 downto 0);  
signal Cin: std_logic;  
begin  
  ...  
  R <= X + Y + Cin;  
  ...  
end architecture;
```



- w -bit adder: connect w FA in series


Ripple-Carry-Adder
 
```
signal R, X, Y: std_logic_vector(w-1 downto 0);  
signal Cin: std_logic;  
begin  
  ...  
  R <= X + Y + Cin;  
  ...  
end architecture;
```




- w -bit adder: connect w FA in series
- $T = \text{delay}_1 + (w - 1)\text{delay}_{C_{out}} + \max(\text{delay}_{C_{out}}, \text{delays})$

Pipeline a w -bit addition: How To ?

 


Pipeline a w -bit addition: How To ?

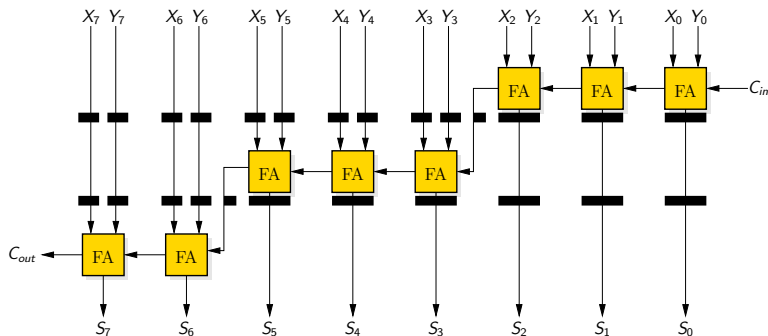


- break carry-propagation path such that $T_{RCA_\alpha} < 1/f$
- $\alpha = \frac{1/f - \text{delay}_1 - \max(\text{delay}_{C_{out}}, \text{delays})}{\text{delay}_{C_{out}}} + 1$
- synchronize I/O using registers \rightarrow **register overhead**

Pipeline a w -bit addition: How To ?

 


- break carry-propagation path such that $T_{RCA_\alpha} < 1/f$
- $\alpha = \frac{1/f - \text{delay}_1 - \max(\text{delay}_{C_{out}}, \text{delays})}{\text{delay}_{C_{out}}} + 1$
- synchronize I/O using registers → **register overhead**

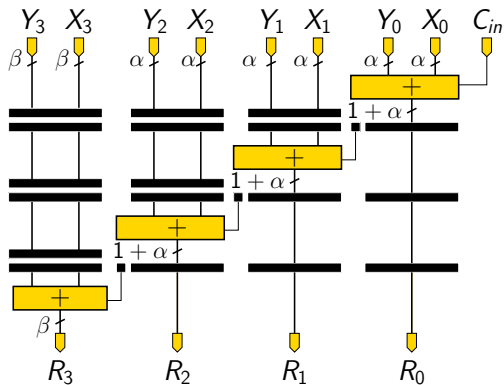Classical Pipelined Addition Architecture



- encountered in literature [EL04, MJE97]
- named also **traditional**

 Classical Pipelined Addition Architecture




- encountered in literature [EL04, MJE97]
- named also **traditional**

How many resources does it take ?


Resource Estimation Techniques

 heterogeneous FPGA: LUTs, Registers, RAM, DSP-blocks etc



Resource Estimation Techniques

 
heterogeneous FPGA: LUTs, Registers, RAM, DSP-blocks etc



- Q: What to count ?
 - Depends on the designer needs
 - In our case we prefer to count the **atomic entities**
 - ▶ Slices on VirtexII, Spartan3, Virtex4 (should be half-slices)
 - ▶ LUTs, Registers on Virtex5

Resource Estimation Techniques

 heterogeneous FPGA: LUTs, Registers, RAM, DSP-blocks etc




- Q: What to count ?
 - Depends on the designer needs
 - In our case we prefer to count the **atomic entities**
 - ▶ Slices on VirtexII, Spartan3, Virtex4 (should be half-slices)
 - ▶ LUTs, Registers on Virtex5

Case Study:


We evaluate the resources required by the classical architecture

Case Study: Classical Architecture

 


- k chunks, w -bit addition: $w = (k - 1)\alpha + \beta$

Case Study: Classical Architecture

 


- k chunks, w -bit addition: $w = (k - 1)\alpha + \beta$
- $L =$

Case Study: Classical Architecture

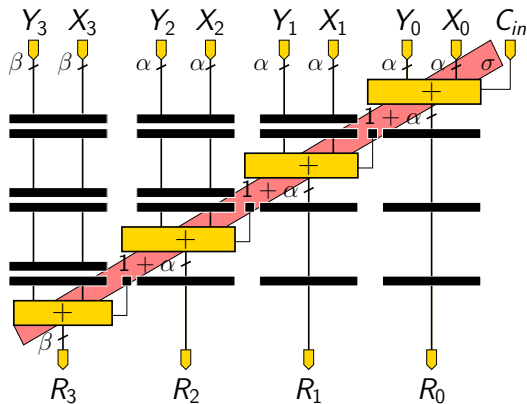


- k chunks, w -bit addition: $w = (k - 1)\alpha + \beta$
- $L = w +$

Case Study: Classical Architecture

 


- k chunks, w -bit addition: $w = (k - 1)\alpha + \beta$
- $L = w + 2(k - 3)\alpha +$

Case Study: Classical Architecture

 


- k chunks, w -bit addition: $w = (k - 1)\alpha + \beta$
- $L = w + 2(k - 3)\alpha + (k - 2)\alpha +$

Case Study: Classical Architecture

 


- k chunks, w -bit addition: $w = (k - 1)\alpha + \beta$
- $L = w + 2(k - 3)\alpha + (k - 2)\alpha + 2\beta$

Case Study: Classical Architecture

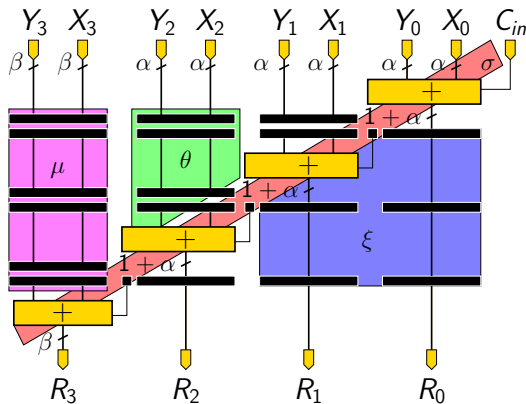


- k chunks, w -bit addition: $w = (k - 1)\alpha + \beta$
- $L = w + 2(k - 3)\alpha + (k - 2)\alpha + 2\beta = w + (3k - 8)\alpha + 2\beta$

Case Study: Classical Architecture

 


- k chunks, w -bit addition: $w = (k - 1)\alpha + \beta$
- $L = w + 2(k - 3)\alpha + (k - 2)\alpha + 2\beta = w + (3k - 8)\alpha + 2\beta$
- $R = (3k - 8)\alpha + 2\beta + \alpha + 2\alpha + k - 1$

Case Study: Classical Architecture

 

- k chunks, w -bit addition: $w = (k - 1)\alpha + \beta$
- $L = w + 2(k - 3)\alpha + (k - 2)\alpha + 2\beta = w + (3k - 8)\alpha + 2\beta$
- $R = (3k - 8)\alpha + 2\beta + \alpha + 2\alpha + k - 1$
- $2S = w + (3k - 8)\alpha + 2\beta + 3\alpha + k - 1 - \alpha$

Alternative Architecture

 

- perform additions as soon as possible
 - propagate carry-out bits for diagonal addition
 - **lower LUT and register consumption** than first version
- Details and formulas in the paper

What If ...

1. operator latency is a problem

What If ...

1. operator latency is a problem

- pipeline depth of previous architectures increase linearly with k
- k increases when f or w increase

What If ...

1. operator latency is a problem

- pipeline depth of previous architectures increase linearly with k
- k increases when f or w increase
- 128-bit addition @ 400MHz, Virtex4 (-12) takes 3 cycles

What If ...

1. operator latency is a problem


- pipeline depth of previous architectures increase linearly with k
- k increases when f or w increase
- 128-bit addition @ 400MHz, Virtex4 (-12) takes 3 cycles

2. no SRL are available

- register count explodes, even for the alternative architecture


Short-Latency Architecture

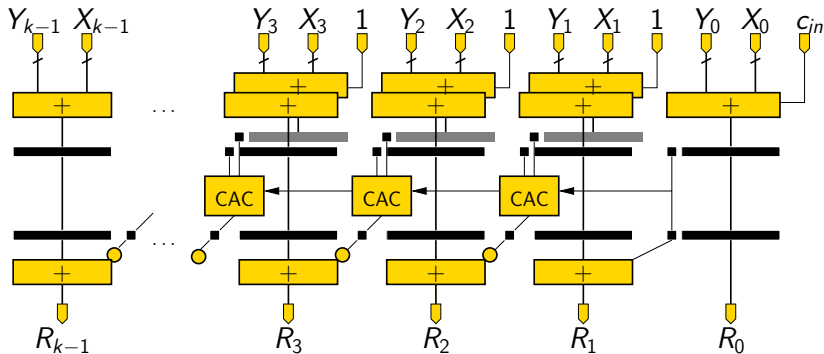- basic idea:
 - perform a **carry-select addition**



Short-Latency Architecture

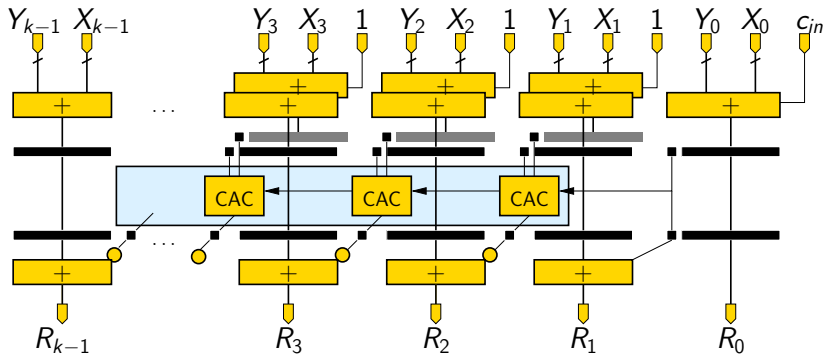
- basic idea:
 - perform a **carry-select addition**
 - use **dedicated fast-carry lines** to speed-up **carry-bit computation**



Short-Latency Architecture: Carry-Adder-Cell

- knowing C_{i-1} , C_i^0 and C_i^1 we compute C_i

$$C_i = f(C_{i-1}, C_i^0, C_i^1)$$

 


C_{i-1}	C_i^0	C_i^1	C_i
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Short-Latency Architecture: Carry-Adder-Cell

- knowing C_{i-1} , C_i^0 and C_i^1 we compute C_i
 
$$C_i : Sum_i = C_{i-1} + C_i^0 + C_i^1$$




C_{i-1}	C_i^0	C_i^1	C_i	Sum_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Short-Latency Architecture: Carry-Adder-Cell

- knowing C_{i-1} , C_i^0 and C_i^1 we compute C_i
 
$$C_i : \neg C_i : Sum_i = C_{i-1} + C_i^0 + C_i^1 + 2$$




C_{i-1}	C_i^0	C_i^1	C_i	$\neg C_i$	Sum_i
0	0	0	0	1	0
0	0	1	0	1	1
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	0	1	1
1	0	1	1	0	0
1	1	0	1	0	0
1	1	1	1	0	1

- portable VHDL that uses fast-carry lines

```
op0 <= "0" & C4_0 & "0" & C3_0 & "0" & C2_0 & "0" & C1_0;  
op1 <= "1" & C4_1 & "1" & C3_1 & "1" & C2_1 & "1" & C1_1;  
--perform the short carry additions  
rawCarrySum <= op0_d1 + op1_d1 + C0;
```


Short-Latency Architecture: Optimization

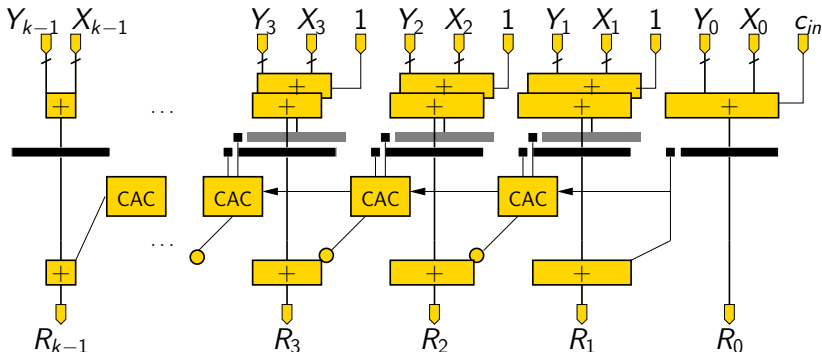- for some values of (w, f) discard second register level



Short-Latency Architecture: Optimization

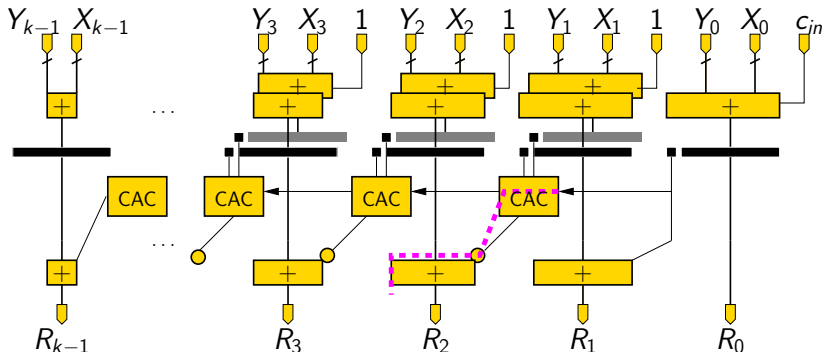
- for some values of (w, f) discard second register level



- greedy algorithm for determining chunk sizes
 - ensure for each chunk: $delay_{CAC} + delay_{routing} + delay_{sum} < 1/f$

Short-Latency Architecture: Optimization

 
- for some values of (w, f) discard second register level



- greedy algorithm for determining chunk sizes
 - ensure for each chunk: $delay_{CAC} + delay_{routing} + delay_{sum} < 1/f$

Short-Latency Architecture: Optimization

 
- for some values of (w, f) discard second register level



- greedy algorithm for determining chunk sizes
 - ensure for each chunk: $delay_{CAC} + delay_{routing} + delay_{sum} < 1/f$


Short-Latency Architecture: Optimization

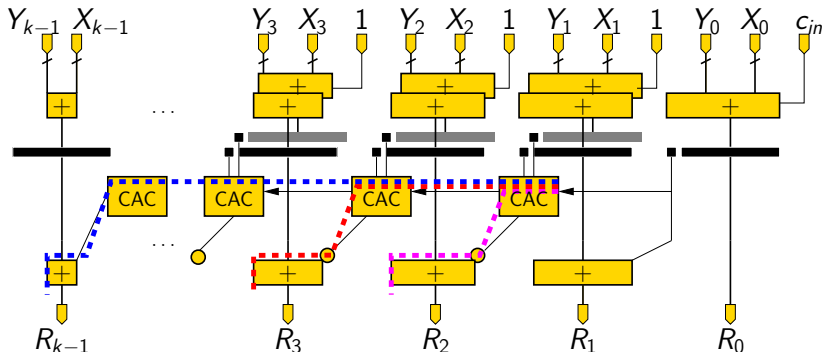- for some values of (w, f) discard second register level




- greedy algorithm for determining chunk sizes
 - ensure for each chunk: $delay_{CAC} + delay_{routing} + delay_{sum} < 1/f$
 - save some registers + 1 cycle count
- if no solution, insert second register level

Reality Check

 


Reality Check

 

Architecture	SRL	Results			Estimations			Mismatch		
		L	R	S	L	R	S	L	R	S
Classical	N	128	573	309	128	573	300	0	0	2%
	Y	318	292	198	318	292	194	0	0	2%
Alternative	N	222	392	216	223	393	207	0.4%	0.2%	4%
	Y	352	199	183	352	199	177	0	0	3%
Short-Latency	N	288	264	216	293	263	214	2%	0.3%	0.9%
	Y	416	136	216	421	137	211	2%	0.7%	2%

Reality Check

 

Architecture	SRL	Results			Estimations			Mismatch		
		L	R	S	L	R	S	L	R	S
Classical	N	128	573	309	128	573	300	0	0	2%
	Y	318	292	198	318	292	194	0	0	2%
Alternative	N	222	392	216	223	393	207	0.4%	0.2%	4%
	Y	352	199	183	352	199	177	0	0	3%
Short-Latency	N	288	264	216	293	263	214	2%	0.3%	0.9%
	Y	416	136	216	421	137	211	2%	0.7%	2%

Largest mismatch 4%: good approximation formulas

Synthesis Results

Size	Freq	Target	SRL	Optim.	Classic.		Altern.		Short-Lat.		Gain ¹
					Cost	D	Cost	D	Cost	D	
32bit	200	Spartan3 (-5)	Y	SLICE	62	4	62	4	76	2	0%
			N		110		84		64		41%
64bit	450	Virtex4 (-12)	Y	SLICE	96	2	81	2	109	2	15%
			N		113		82		110		27%
128bit	450	Virtex4 (-12)	Y	SLICE	247	5	230	5	258	2	6%
			N		516		369		258		50%
128bit	450	Virtex5 (-3)	Y	REG	322	4	232	4	143	2	56%
			N		718		525		267		63%

- proposed architectures gain(for examples):
 - 15% less slices, 56% less registers when SRL
 - 50% less slices, 63% less registers when NO SRL

¹compared to the classical implementation

Conclusions

- binary addition pervasive in FPGA applications
- adder operator generator implemented in FloPoCo
- classical pipeline, plus two novel pipelined addition architectures
- selection of the best implementation given the specifications by accurate resource estimation
- performance and resource improvements for operators using it

Conclusions

- binary addition pervasive in FPGA applications
- adder operator generator implemented in FloPoCo
- classical pipeline, plus two novel pipelined addition architectures
- selection of the best implementation given the specifications by accurate resource estimation
- performance and resource improvements for operators using it

In 2010 we can still improve elementary arithmetic operations on FPGA!

Future Work

- applicable to Altera targets, but need different resource estimation formulas
- low-latency architecture could be improved if synthesis tools were more clever
- implement similar resource evaluation for larger components

Future Work

- applicable to Altera targets, but need different resource estimation formulas
- low-latency architecture could be improved if synthesis tools were more clever
- implement similar resource evaluation for larger components

On-going work on "pipelining made easy" in FloPoCo

Thank you for your attention !

- try it at

<http://www.ens-lyon.fr/LIP/Arenaire/Ware/FloPoCo/>

New release 2.1.0 from Aug. 10, 2010

- or, come to us and ask for a demo

- [DP96] L. Dadda and V. Piuri.
Pipelined Adders.
Computers, IEEE Transactions on, 45(3):348–356, Mar 1996.
- [EL04] M. D. Ercegovac and T. Lang.
Digital Arithmetic.
Morgan Kaufmann Publishers, 2004.
- [MJE97] Peiro Marcos Martinez, Valls Javier, and Boemo Eduardo.
On the design of FPGA-based Multioperand Pipeline Adders.
In *XII Design of Circuits and Integrated System Conference*,
1997.
- [Mul89] J. M. Muller.
Arithmétique des Ordinateurs.
Masson, Paris, 1989.
- [US93] I.H. Unwala and E.E. Swartzlander.
Superpipelined Adder Designs.
In *Circuits and Systems, 1993., ISCAS '93, 1993 IEEE International Symposium on*, pages 1841–1844, May 1993.

- [XY98] Shanzhen Xing and William W.h. Yu.
FPGA Adders: Performance Evaluation and Optimal Design.
IEEE Design and Test of Computers, 15:24–29, 1998.